

Chapter 10. Sinusoidal Steady-state Analysis


1. Forced response to sinusoidal source
2. Complex forcing function and **Phasor**
3. AC circuit analysis using Phasor
4. Phasor diagram

회로이론-2.10 Sinusoidal Steady-State Analysis

1

Sinusoids 정현파

- $v(t) = V_m \cdot \sin \omega t$

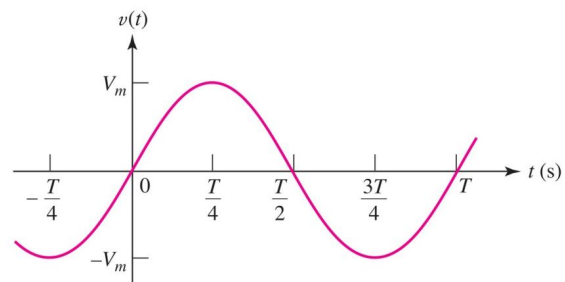


- ✓ Amplitude or magnitude, $V_m > 0$
- ✓ Angular frequency, $\omega = 2\pi f \left[\frac{\text{rad}}{\text{sec}} \right]$, frequency $f \text{ [Hz]}$
- ✓ Periodic with period $T = 1/f$

회로이론-2.10 Sinusoidal Steady-State Analysis

10-2

Phase of Sin Wave

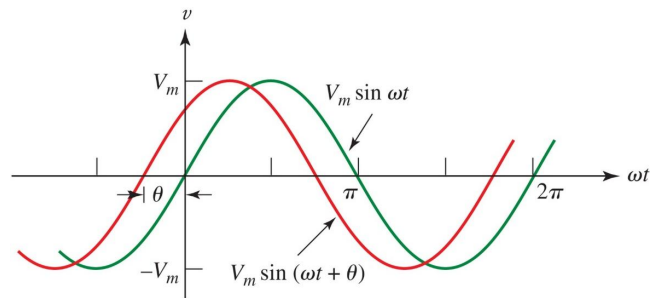- $v_1(t) = V_m \cdot \sin(\omega t + \theta)$



✓ $v_1(t)$ **leads** $v_0(t) = V_m \cdot \sin \omega t$ by θ .

✓ $v_0(t)$ **lags** $v_1(t)$ by θ .

✓ $V_m \cdot \sin(\omega t + \theta_1)$ and $V_m \cdot \sin(\omega t + \theta_2)$ are in-phase (동상), if $\theta_1 = \theta_2$.

† Out-of-phase, if $\theta_1 \neq \theta_2$

- **Example:** $v_1(t) = V_{m1} \cdot \cos(5t + 10^\circ)$ and $v_2(t) = V_{m2} \cdot \sin(5t - 30^\circ)$

✓ $v_1(t)$ leads $v_2(t)$ by 130° .

✓ $\sin \omega t = \cos(\omega t - 90^\circ)$

Phasor Diagram

- Given $v_1(t) = V_{m1} \cdot \cos(5t + 10^\circ)$ and $v_2(t) = V_{m2} \cdot \sin(5t - 30^\circ)$

✓ Graphical representation of two sinusoids $v_1(t)$ and $v_2(t)$

† Amplitude and phase information:


– Vector notation, **phasor**, v_1 and v_2

† Only possible when they have the **same frequency**.

† Leading/lagging is determined by the angular difference between two vectors in CW direction.

– v_2 leads v_1 by 130° .


– v_1 lags v_2 by 130° .

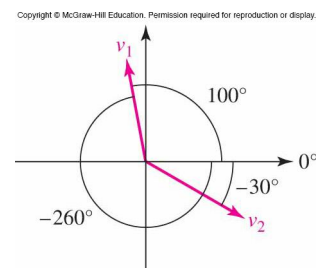

Forced Response to Sine Sources

- Steady-state response of RL series circuit to the sinusoidal source
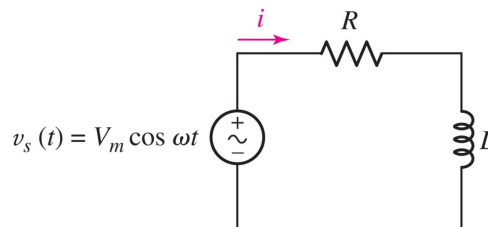
$$v_s(t) = V_m \cdot \cos \omega t, -\infty < t < \infty$$



$$\text{KVL: } L \frac{di}{dt} + Ri = v_s(t)$$

$$\text{Choose } i(t) = A \cdot \cos \omega t + B \cdot \sin \omega t$$

† Method of undetermined coefficient, 미정 계수법

$$i(t) = \frac{RV_m}{R^2 + \omega^2 L^2} \cos \omega t + \frac{\omega LV_m}{R^2 + \omega^2 L^2} \sin \omega t$$

Forced Response to Sine Sources

- If $i(t) = a \cdot \cos \omega t + b \cdot \sin \omega t$,

$$i(t) = \sqrt{a^2 + b^2} \left(\frac{a}{\sqrt{a^2 + b^2}} \cos \omega t + \frac{b}{\sqrt{a^2 + b^2}} \sin \omega t \right) = \sqrt{a^2 + b^2} \cos(\omega t - \theta)$$

$$\text{† where } \theta = \tan^{-1} \left(\frac{b}{a} \right)$$

- In the RL series circuit,

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cdot \cos \left(\omega t - \tan^{-1} \frac{\omega L}{R} \right)$$

† Current $i(t)$ lags the source voltage $v_s(t)$ by $\theta = \tan^{-1} \left(\frac{\omega L}{R} \right)$, $0^\circ < \theta < 90^\circ$.

In a linear circuit with sinusoidal source, every circuit variables (currents as well as voltages) are sinusoids with the same angular frequency as the source.

Steady-State Response


• Example 10.1 Find $i_L(t)$.

✓ Thevenin equivalent seen from terminals $a - b$ (or from the inductor):




$$✓ v_{oc} = v_s(t) \cdot \frac{100}{100+25} = 8 \cdot \cos 10^3 t \text{ and } R_{th} = 25 \parallel 100 = 20 [\Omega]$$

$$✓ i_L(t) = \frac{8}{\sqrt{20^2 + 10^6 \cdot 9 \times 10^{-4}}} \cdot \cos(10^3 t - \tan^{-1} \frac{30}{20})$$
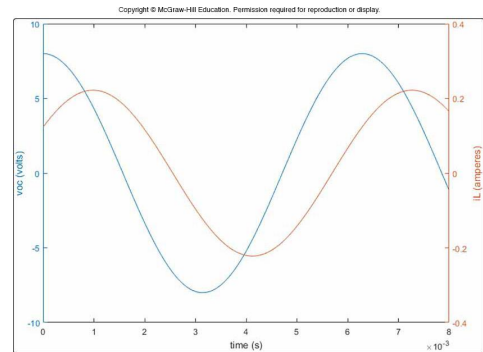
$$+ i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cdot \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$



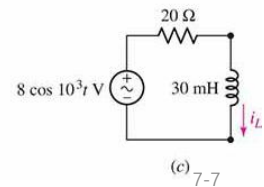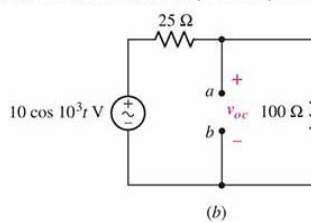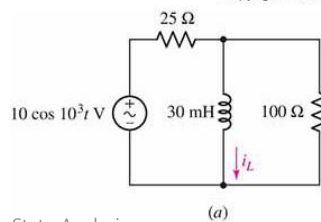
Copyright © McGraw-Hill Education. Permission required for reproduction or display.



회로이론-2.10 Sinusoidal Steady-State Analysis



Complex Forcing Function
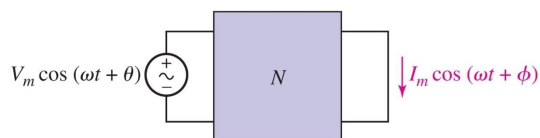
$$• v_s(t) = V_m \cdot e^{j(\omega t + \theta)} = V_m \cdot \cos(\omega t + \theta) + jV_m \cdot \sin(\omega t + \theta)$$



Assume response $i(t) = I_m \cdot \cos(\omega t + \phi)$ when $v_s(t) = V_m \cdot \cos(\omega t + \theta)$
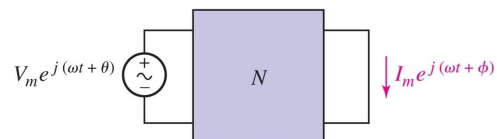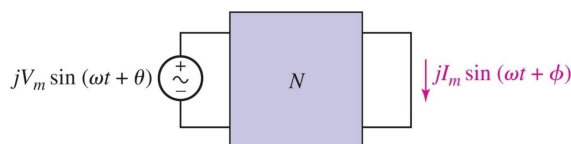
$$✓ V_m \cdot \sin(\omega t + \theta) = V_m \cdot \cos(\omega t + \theta - 90^\circ) \rightarrow I_m \cdot \cos(\omega t + \phi - 90^\circ) = I_m \cdot \sin(\omega t + \phi)$$



Real part of complex response is generated by the real part of the complex forcing function, and so is the imaginary part.

회로이론-2.10 Sinusoidal Steady-State Analysis

10-8


Steady-State Response to Complex Source

- Consider a series RL circuit with $v_s(t) = V_m \cdot e^{j\omega t}$
 - $\checkmark L \frac{di}{dt} + Ri = V_m \cdot e^{j\omega t}$
 - \checkmark Choose $i(t) = I_m \cdot e^{j(\omega t + \phi)}$ ($= I_m e^{j\phi} \cdot e^{j\omega t}$)
 - $\dagger j\omega L I_m e^{j(\omega t + \phi)} + R I_m e^{j(\omega t + \phi)} = V_m \cdot e^{j\omega t}$
 - $\dagger j\omega L I_m e^{j\phi} + R I_m e^{j\phi} = V_m \Rightarrow I_m e^{j\phi} (j\omega L + R) = V_m$
 - $\dagger I_m e^{j\phi} = \frac{V_m}{R + j\omega L} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \exp\left\{-j \tan^{-1}\left(\frac{\omega L}{R}\right)\right\} = I_m \angle \phi$ (polar notation: phasor)
 - $\dagger I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$ and $\phi = -\tan^{-1}\left(\frac{\omega L}{R}\right)$
 - \checkmark Response to the source $v_s(t) = V_m \cdot \cos \omega t$ is then
 - $\dagger i(t) = I_m \cdot \cos(\omega t + \phi) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cdot \cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right)$

Steady-State Response

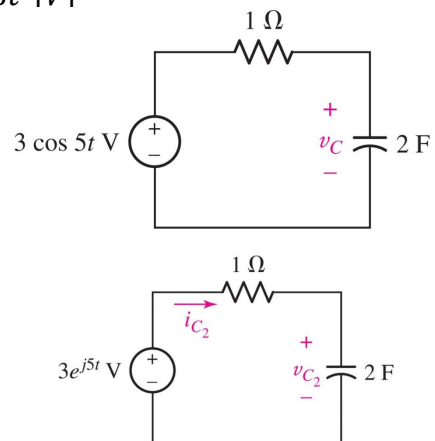- Example 10.2** Find $v_c(t)$, when $v_s(t) = 3 \cdot \cos 5t$ [V]

- \checkmark Circuit equation:
 - $\dagger 2 \frac{dv_c}{dt} = v_s(t) - v_c(t)$
- \checkmark Equation with **exponential source**
 - $\dagger 2 \frac{dv_{ce}}{dt} = 3e^{j5t} - v_{ce}(t)$, where $v_{se}(t) = 3e^{j5t}$
- \checkmark Let $v_{ce}(t) = V_m e^{j5t}$ (much easier to solve)
 - $\dagger V_m = \frac{3}{1 + j10} = \frac{3}{\sqrt{1+100}} \angle -\tan^{-1} 10$
- $\checkmark v_c(t) = \text{Re}\{v_{ce}(t)\} = 29.85 \cos(5t - 84.3^\circ)$



Phasor

In a linear circuit, every circuit variables with sinusoidal input is **sinusoid with the same angular frequency as the source**. Thus, they can be represented by their **magnitude and phase** only, known as **phasor**.

✓ The term $e^{j\omega t}$ is common to all circuit variables:

† Guaranteed in the method of undetermined coefficients

✓ Phasor

sinusoidal function	complex function	phasor
$v(t) = V_m \cos \omega t$	$v_c(t) = V_m e^{j\omega t}$	$\mathbf{V} = V_m \angle 0^\circ$
$i(t) = I_m \cos(\omega t + \phi)$	$i_c(t) = I_m e^{j(\omega t + \phi)}$	$\mathbf{I} = I_m \angle \phi$

† $i(t) = I_m \cos(\omega t + \phi) = \text{Re}\{I_m e^{j(\omega t + \phi)}\} = \text{Re}\{\mathbf{I} e^{j\omega t}\}$

† Phasor representation of a voltage (or current) is a **frequency-domain representation**.

Phasor

• Example 10.3

✓ $v_a(t) = 100 \cos(400t - 30^\circ)$, $\mathbf{V}_a = 100 \angle -30^\circ$


✓ $v_b(t) = -5 \sin(580t - 110^\circ) = -5 \cos(580t - 200^\circ) = 5 \cos(580t - 20^\circ)$

$\mathbf{V}_b = 5 \angle -20^\circ$

✓ $v_c(t) = 3 \cos(4t - 30^\circ) + 4 \sin(4t - 100^\circ) = 3 \cos(4t - 30^\circ) + 4 \cos(4t + 170^\circ)$

$\mathbf{V}_c = 3 \angle -30^\circ + 5 \angle 170^\circ$

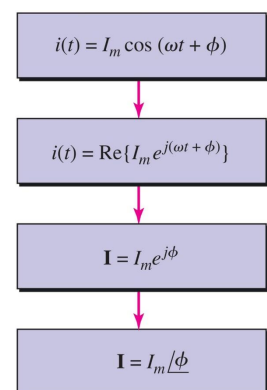$\mathbf{V}_c = (2.5981 - j1.5) + (-4.9240 + j.8682) = -2.326 - j.6318 = 2.4102 \angle -164.8044^\circ$



Phasor: Resistor


- Phasor in resistor

- ✓ $v(t) = Ri(t)$

- ✓ When $i(t) = I_m e^{j(\omega t + \theta)}$, $v(t) = RI_m e^{j(\omega t + \theta)}$

- ✓ $\mathbf{V} = R\mathbf{I}$, where $\mathbf{I} = I_m e^{j\theta}$

- ✓ $R = \frac{\mathbf{V}}{\mathbf{I}}$

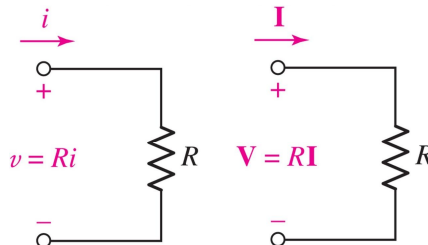

Phasor: Inductor

- Phasor in inductor


- ✓ $v(t) = L \frac{di(t)}{dt}$

- ✓ When $i(t) = I_m e^{j(\omega t + \phi)}$, $v(t) = LI_m \cdot j\omega \cdot e^{j(\omega t + \phi)} = j\omega LI_m e^{j(\omega t + \phi)}$

- ✓ $\mathbf{V} = j\omega L\mathbf{I}$, where $\mathbf{I} = I_m e^{j\phi}$

- ✓ $Z_L = \frac{\mathbf{V}}{\mathbf{I}} = j\omega L$

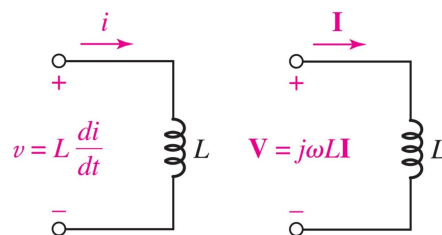† Differentiation in time becomes multiplication in phasor form.



Phasor: Capacitor


- Phasor in capacitor

$$i(t) = C \frac{dv(t)}{dt}$$

$$\text{When } v(t) = V_m e^{j(\omega t + \theta)}, i(t) = j\omega C V_m e^{j(\omega t + \theta)}$$

$$I = j\omega C V, \text{ where } V = V_m e^{j\theta}$$
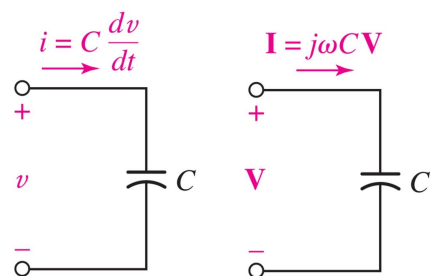
$$Z_c = \frac{V}{I} = \frac{1}{j\omega C}$$




회로이론-2.10 Sinusoidal Steady-State Analysis

10-15


Phasor: Voltage/current relationship

Time Domain

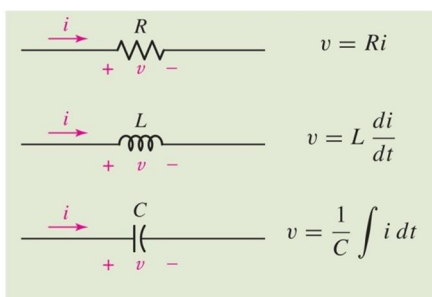

Calculus (hard but real)

Phasor (frequency domain)

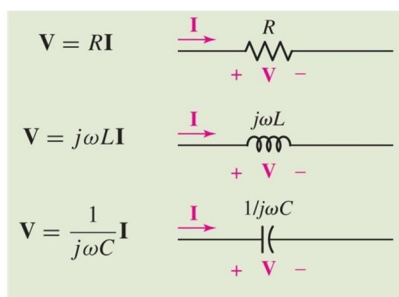

Algebra (easy but complex)

회로이론-2.10 Sinusoidal Steady-State Analysis

10-16

KVL & KCL

- KVL: $\mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_N = \mathbf{0}$ and KCL: $\mathbf{I}_1 + \mathbf{I}_2 + \cdots + \mathbf{I}_N = \mathbf{0}$


- Example: RL series circuit

$$\checkmark v_R(t) + v_L(t) = v_s(t)$$

$$\checkmark \mathbf{V}_R + \mathbf{V}_L = \mathbf{V}_S$$

$$\checkmark R\mathbf{I} + j\omega L\mathbf{I} = \mathbf{V}_S$$
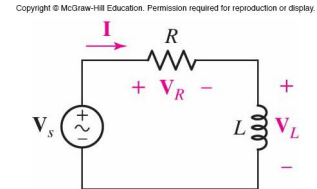
$$\checkmark I = \frac{\mathbf{V}_S}{R + j\omega L} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$



Circuit Analysis with Phasor

- Example 10.5 Find $i_s(t)$, when $\omega = 2[\text{rad/s}]$ and $\mathbf{I}_C = 2\angle -28^\circ$.


$$\checkmark \mathbf{V}_C = \frac{1}{j\omega C} \mathbf{I}_C = 1 e^{-j62^\circ} \text{ (exponents are usually written in [rad])}.$$

$$\checkmark \mathbf{I}_{R2} = \frac{1}{2} \mathbf{V}_C$$

$$\checkmark \mathbf{I}_S = \mathbf{I}_{R2} + \mathbf{I}_C = \frac{1}{2} (\cos(-62^\circ) + j \sin(-62^\circ)) + 2(\cos(-28^\circ) + j \sin(-28^\circ))$$

$$\mathbf{I}_S = (.2347 - j.4415) + (1.7659 - j.9389) = 2.0 - j1.3804 = 2.4307\angle -34.6053^\circ$$
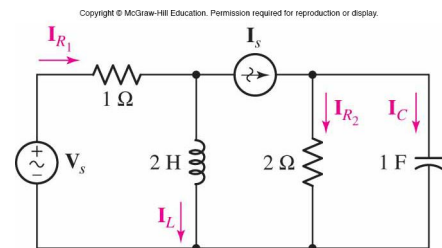
$$\checkmark i_s(t) = 2.4307 \cos(2t - 34.6053^\circ)$$



Impedance

- Impedance, $\mathbf{Z} = \mathbf{V}/\mathbf{I}$

- ✓ $\mathbf{V} = R\mathbf{I}$, $\mathbf{V} = j\omega L\mathbf{I}$, $\mathbf{V} = \frac{1}{j\omega C}\mathbf{I}$: $\mathbf{Z}_R = R$, $\mathbf{Z}_L = j\omega L$, and $\mathbf{Z}_C = \frac{1}{j\omega C}$

- † Impedance is the equivalent of resistance in phasor (frequency domain).

- † Impedance is a complex number.

- † Impedance in series/parallel can be combined as resistance.

- Example

- ✓ Series connection of a inductor ($L = 5 \text{ [mH]}$) and a capacitor ($C = 100 \text{ [\mu F]}$) at $\omega = 10^4 \text{ [rad/s]}$

- ✓ $\mathbf{Z}_S = \mathbf{Z}_L + \mathbf{Z}_C = j(10^4)(5 \times 10^{-3}) + \frac{1}{j(10^4)(100 \times 10^{-6})} = j49 \text{ [\Omega]}$

- ✓ If parallel, $\mathbf{Z}_p = \mathbf{Z}_L || \mathbf{Z}_C = \mathbf{Z}_L | \mathbf{Z}_C = \frac{\mathbf{Z}_L \mathbf{Z}_C}{\mathbf{Z}_L + \mathbf{Z}_C} = \frac{50}{j49} \text{ [\Omega]}$

Admittance & Reactance

- Admittance, $\mathbf{Y} = \frac{1}{\mathbf{Z}}$

- ✓ $\mathbf{Y}_R = \frac{1}{R}$, $\mathbf{Y}_L = \frac{1}{j\omega L}$, and $\mathbf{Y}_C = j\omega C$

- If $\mathbf{Z} = R + jX$ (rectangular form)

- ✓ R ... resistance

- ✓ X ... reactance [Ω]

- If $\mathbf{Y} = G + jB$

- ✓ G ... conductance

- ✓ B ... susceptance [S, Siemen]

Combination of Impedance

• Example 10.6 $\omega = 5 \text{ [rad/s]}$

$$\checkmark 6 \parallel (-j0.4) = \frac{-j2.4}{6-j0.4} = \frac{-j2.4}{6.0133 \angle -0.0666} = 0.3991 \angle -1.5042$$

$$\text{or } .02655 - j.3982$$



✓ Series connection of 2 [H] , 200 [mF] and $6 \text{ [}\Omega\text{]} \parallel 500 \text{ [mF]}$

$$-j + j10 + .0265 - j.3982 = .02655 + j8.602$$

✓ Parallel connection to $10 \text{ [}\Omega\text{]}$

$$(.02655 + j8.602) \parallel 10 = \frac{.2655 + j86.02}{10.02655 + j8.602} = 4.255 + j4.929$$
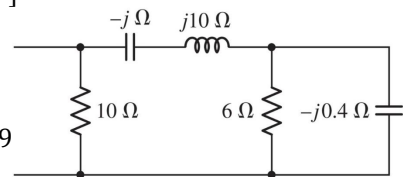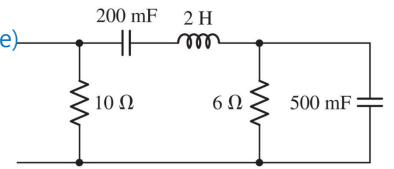
$$\text{or } 6.511 \angle 49.20^\circ \text{ [}\Omega\text{]}$$



Circuit Analysis with Phasor


• Example 10.7 Find $i(t)$.

$$\checkmark \mathbf{Z}_{eq} = 1.5 + (1 - j2) \parallel j = 1.5 + \frac{2+j}{1-j} = 1.5 + \frac{1+j3}{2} = 2 + j1.5 = 2.5e^{j36.87^\circ},$$


$$\checkmark \mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}_{eq}} = 16e^{-j126.9^\circ}$$

$$\checkmark i(t) = 16 \cos(3000t - 126.9^\circ) \text{ [mA]}$$

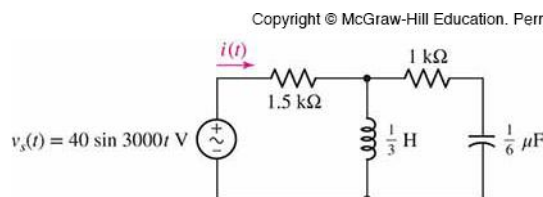† Impedance seen from the source is **inductive** (Positive phase in \mathbf{Z}_{eq}).



(a)

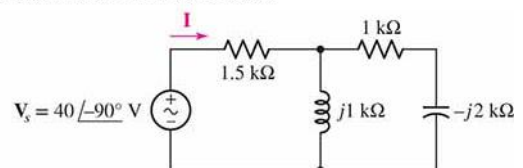

(b)

Nodal Analysis with Phasor

• Example 10.8 Find $v_1(t)$.


✓ Phasor node voltages \mathbf{V}_1 and \mathbf{V}_2 .

$$\frac{\mathbf{V}_1}{5} + \frac{\mathbf{V}_1}{-j10} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j10} = 1, \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j5} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{j10} + \frac{\mathbf{V}_2}{j5} + \frac{\mathbf{V}_2}{10} = j0.5$$

✓ $(0.2 + j0.2)\mathbf{V}_1 - j0.1\mathbf{V}_2 = 1$ and $-j0.1\mathbf{V}_1 + (0.1 - j0.1)\mathbf{V}_2 = j0.5$

✓ $\mathbf{V}_1 = 1 - j2 = 2.24\angle -63.4^\circ$ and $\mathbf{V}_2 = -2 + j4 = 4.47\angle 116.6^\circ$ [V]

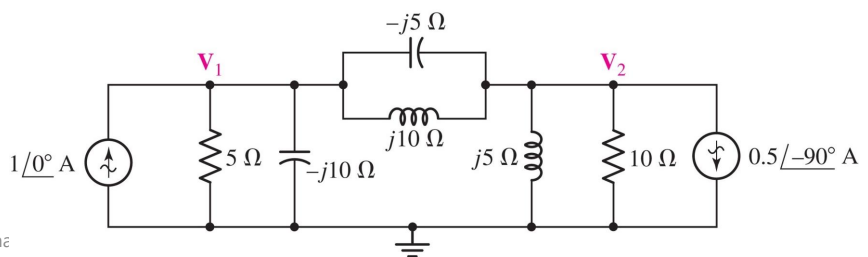✓ $v_1(t) = 2.24 \cos(\omega t - 63.4^\circ)$ and $v_2(t) = 4.47 \cos(\omega t + 116.6^\circ)$



회로이론-2.10 Sinusoidal Steady-State Analysis

Mesh Analysis with Phasor

• Example 10.9 Find $i_1(t)$.

✓ Phasor mesh currents \mathbf{I}_1 and \mathbf{I}_2 .

$$3\mathbf{I}_1 + j4(\mathbf{I}_1 - \mathbf{I}_2) = 10 \text{ or } (3 + j4)\mathbf{I}_1 - j4\mathbf{I}_2 = 10 \quad 10 \cos 10^3 t \text{ V}$$



$$3\mathbf{I}_1 + j4(\mathbf{I}_2 - \mathbf{I}_1) - j2\mathbf{I}_2 + 2\mathbf{I}_1 = 0 \text{ or}$$

$$(2 - j4)\mathbf{I}_1 + j2\mathbf{I}_2 = 0$$

$$\mathbf{I}_1 = \frac{14 + j8}{13} = 1.24\angle 29.7^\circ \text{ and } \mathbf{I}_2 = \frac{20 + j30}{13} = 2.77\angle 56.3^\circ$$

✓ $i_1(t) = 1.24 \cos(\omega t + 29.7^\circ)$ and
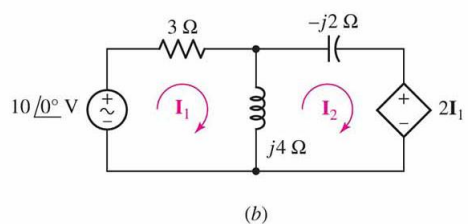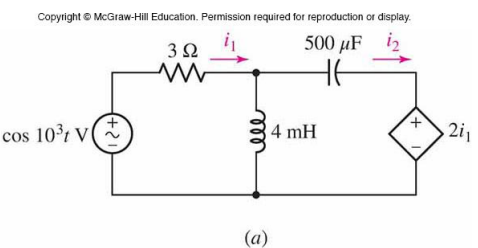
$$i_2(t) = 2.77 \cos(\omega t + 56.3^\circ)$$



회로이론-2.10 Sinusoidal Steady-State Analysis

Superposition with Phasor

- Example 10.10 Find $v_1(t)$.



$$v_1 = v_{1L} + v_{1R}$$

$$v_{1L} = \frac{(4-j2) \cdot (-j10+2+j4)}{(4-j2)+(-j10+2+j4)} 1 \angle 0^\circ = 2 - j2$$

$$v_{1R} = \frac{2+j4}{(4-j2)+(-j10+2+j4)} (-0.5 \angle -90^\circ) = -1$$

$$v_1 = 1 - j2 [V]$$
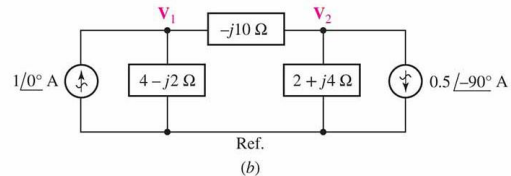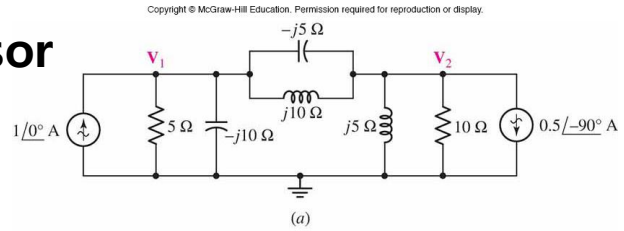
$$v_1(t) = 2.24 \cos(\omega t - 63.4^\circ)$$






Thevenin with Phasor

- Example 10.11 Find the Thevenin equivalent circuit seen from $-j10$.

$$v_{oc} = (1 \angle 0^\circ) \cdot (4 - j2) - (-0.5 \angle -90^\circ)(2 + j4) [V]$$

$$z_{th} = (4 - j2) + (2 + j4) = 6 + j2, I_{12} = \frac{6-j3}{(6+j2)-j10} = 0.6 + j0.3 [A]$$

$$I_1 = 1 - (0.6 + j0.3) [A]$$

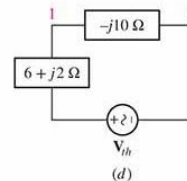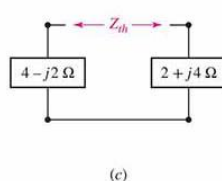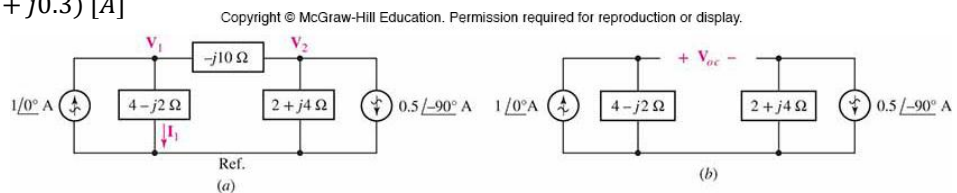


Thevenin with Phasor

- **Example 10.12** Two sources with different frequencies.

$$\checkmark \mathbf{I}' = (2\angle 0^\circ) \cdot \frac{-j0.4}{10-j-j0.4} = 79.23\angle -82.03^\circ [\text{mA}], i'(t) = 79.23 \cos(5t - 82.03^\circ)$$

$$\checkmark \mathbf{I}'' = (5\angle 0^\circ) \cdot \frac{-j1.667}{10-j0.6667-j1.667} = 811.7\angle -76.86^\circ [\text{mA}]$$
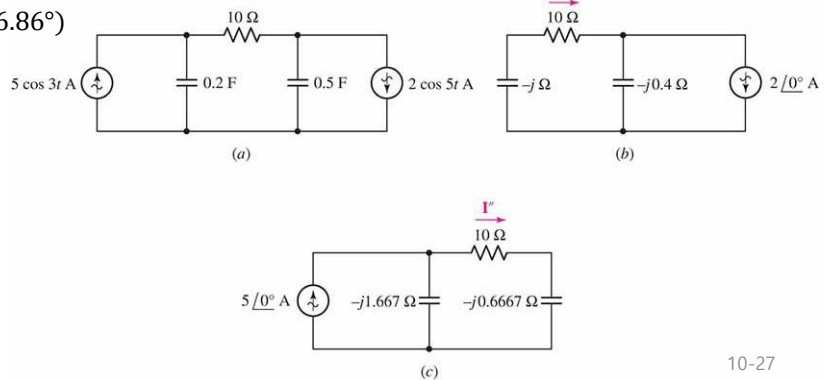
$$\checkmark i''(t) = 811.7 \cos(3t - 76.86^\circ)$$



회로이론-2.10 Sinusoidal Steady-State Analysis


10-27

Phasor Diagram

- Complex phasor as a vector in the complex plane

$$\checkmark \mathbf{V}_1 = 6 + j8 = 10\angle 53.1^\circ [\text{V}]$$

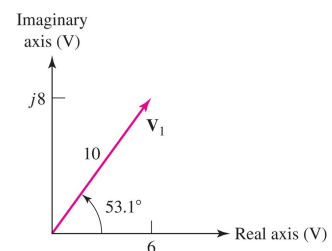
† $v(t)$... projection onto the real axis



- ✓ Phasor addition, $\mathbf{V}_1 + \mathbf{V}_2 =$ vector addition

- ✓ vi -relation as phasors
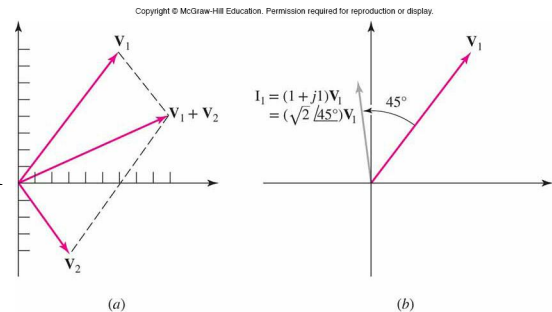
$$\mathbf{I}_1 = \mathbf{Y}\mathbf{V}_1, \text{ with } \mathbf{I}_1 = (1+j)\mathbf{V}_1 = (\sqrt{2}\angle 45^\circ)\mathbf{V}_1$$



회로이론-2.10 Sinusoidal Steady-State Analysis

10-28

Phasor Diagram: Parallel RLC Circuit

- Example:

- ✓ Given $\mathbf{V} = 1\angle 0^\circ$ [V]

- ✓ $\mathbf{I}_R = 0.2\angle 0^\circ$ [A]

- ✓ $\mathbf{I}_L = 0.1\angle -90^\circ$ [A]

- ✓ $\mathbf{I}_C = 0.3\angle 90^\circ$ [A]

- † $\mathbf{I}_x = \mathbf{I}_R + \mathbf{I}_L = 0.2 - j0.1 = 0.224\angle -26.6^\circ$ [A]

- † $\mathbf{I}_S = \mathbf{I}_x + \mathbf{I}_C = 0.283\angle 45^\circ$ [A]

- † \mathbf{I}_S leads \mathbf{I}_S by 45° , \mathbf{I}_C by -45° , and \mathbf{I}_x by 71.6° .

- † Angles are relative to the voltage phasor.

