

Chapter 15. Frequency Response

1. Transfer Function
2. Bode Diagram
3. Parallel Resonance
4. Bandwidth
5. Series Resonance

회로이론-2. 15. Frequency Response

15-1

Transfer Function & Frequency Response

• Frequency response, $H(j\omega) = |H(j\omega)|\angle\phi(j\omega)$

• Example 15.1 RC circuit

$$\checkmark V_{out} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in} \text{ (phasor form)}$$




$$\checkmark V_{out}(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in}(j\omega)$$

$$\checkmark \text{Frequency response, } H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{1 + j\omega/\omega_0}$$

$$\dagger \omega_0 = \frac{1}{RC} \text{ (natural frequency)}$$

$$\dagger |H(j\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}} \text{ and}$$
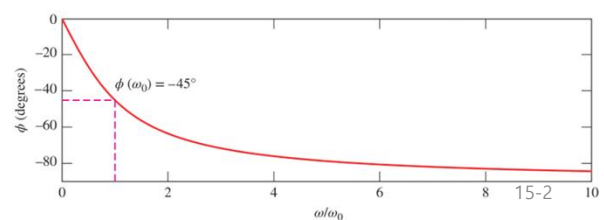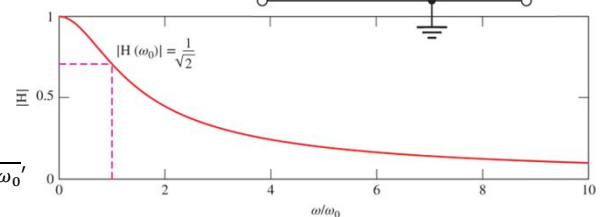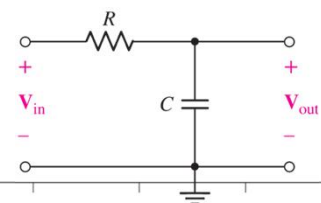
$$\dagger \angle H(j\omega) = \phi(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$



회로이론-2. 15. Frequency Response

Bode Diagram

- Bode plot ... Approximate visual plot of frequency response

✓ Magnitude and phase plot on a logarithmic scale of frequency, ω

✓ Magnitude, $H_{dB} = 20 \cdot \log_{10}|H(j\omega)|$

† $|H(j\omega)| = 10^{H_{dB}/20}$

- dB values

✓ $\log_{10} 1 = 0, \log_{10} 2 = 0.3, \log_{10} 10 = 1$

† $20 \cdot \log_{10} 1 = 0, 20 \cdot \log_{10} 2 = 6, 20 \cdot \log_{10} 10 = 20, 20 \cdot \log_{10} 10^n = 20n \text{ [dB]}$

† $20 \cdot \log_{10} 0.1 = -20, 20 \cdot \log_{10} \frac{1}{\sqrt{2}} = -3 \text{ [dB]}$

✓ When $|H(j\omega)|$ increases 2-times, H_{dB} increases 6 [dB].

† 10-fold increase on $|H(j\omega)| \Rightarrow 20 \text{ [dB]}$ increase in H_{dB} .

† 10^n times increase on $|H(j\omega)| \Rightarrow 20n \text{ [dB]}$ increase in H_{dB} .

Asymptote 점근선

- Simple zero at $s = 0$

✓ $H(s) = 1 + \frac{s}{a}$ or $H(j\omega) = 1 + \frac{j\omega}{a}$

✓ $|H(j\omega)| = \sqrt{1 + \frac{\omega^2}{a^2}}, H_{dB} = 20 \cdot \log_{10} \sqrt{1 + \frac{\omega^2}{a^2}}$

† If $\omega \ll a, |H(j\omega)| \approx 20 \cdot \log_{10} 1 = 0$


† If $\omega \gg a, |H(j\omega)| \approx 20 \cdot \log_{10} \frac{\omega}{a} \dots$

– asymptote with **20 [dB/decade]** or **6 [dB/octave]**

† When $\omega = a,$

– $|H(j\omega)|_{\omega=a} = \sqrt{2}, H_{dB}|_{\omega=a} = 3 \text{ [dB]}$

– **corner, 3 dB, half-power frequency**

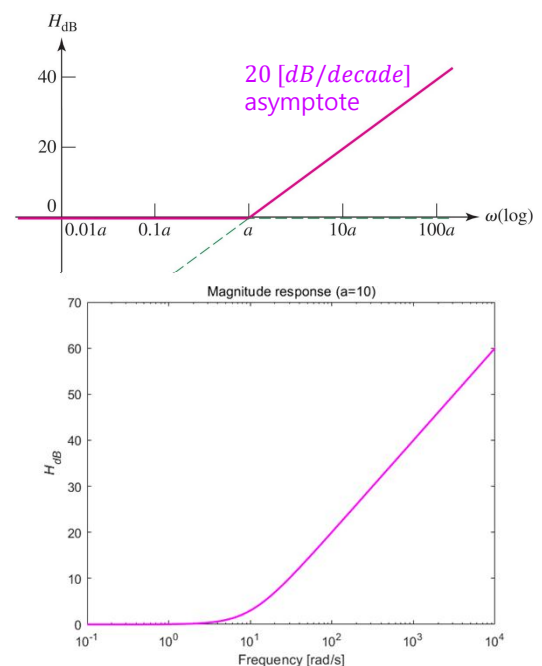

Asymptote 2

- Two simple zeros



$$\checkmark H(s) = K \left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_2}\right)$$

$$\checkmark H_{dB} = 20 \cdot \log_{10} \left| K \left(1 + \frac{j\omega}{\omega_1}\right) \left(1 + \frac{j\omega}{\omega_2}\right) \right| \text{ or}$$

$$\checkmark H_{dB} = 20 \cdot \log K + 20 \cdot \log \sqrt{1 + \frac{\omega^2}{\omega_1^2}} + 20 \cdot \log \sqrt{1 + \frac{\omega^2}{\omega_2^2}}$$

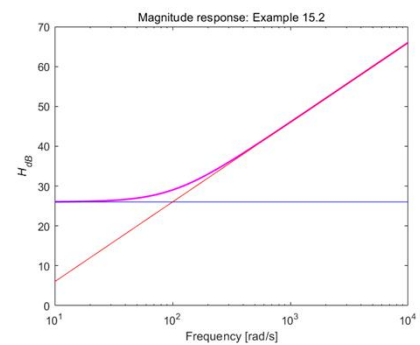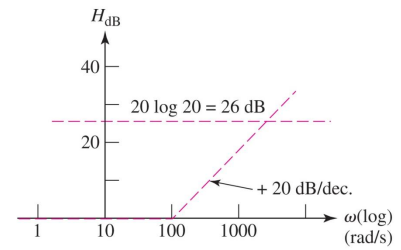- Example 15.2 $H(s) = Z_{in}(s) = 20 + 0.2s$

$$\checkmark H(s) = 20 \left(1 + \frac{s}{100}\right)$$



회로이론-2. 15. Frequency Response

15-5

Asymptote 3

- Simple pole at $s = -a$

$$\checkmark H(s) = \frac{1}{1+s/a} \text{ or } H(j\omega) = \frac{1}{1+j\omega/a}$$

$$\checkmark |H(j\omega)| = \left(1 + \frac{\omega^2}{a^2}\right)^{-1/2}$$


$$\checkmark H_{dB} = 20 \cdot \log_{10} \left(1 + \frac{\omega^2}{a^2}\right)^{-1/2} = -10 \cdot \log_{10} \left(1 + \frac{\omega^2}{a^2}\right)$$

$$\dagger \text{ If } \omega \ll a, |H(j\omega)| \approx 0$$

$$\dagger \text{ If } \omega \gg a, |H(j\omega)| \approx -20 \cdot \log_{10} \frac{\omega}{a}$$

– asymptote with -20 [dB/decade]
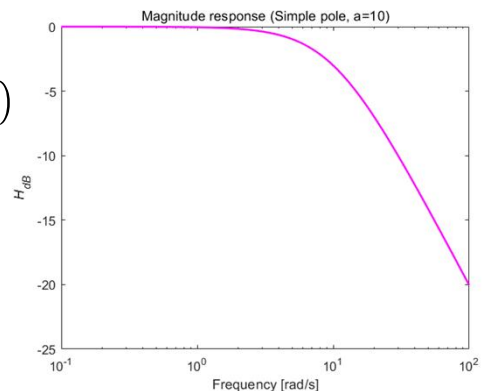
$$\dagger \text{ When } \omega = a, H_{dB} = -3 \text{ [dB]}$$



회로이론-2. 15. Frequency Response

15-6

Asymptote 4

• Complex conjugate zeros

$$\checkmark H(s) = 1 + 2\zeta \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2$$

† When $0 \leq \zeta < 1$ ($\zeta = \frac{\alpha}{\omega_a}$, **damping factor**),
complex conjugate zeros.


$$\checkmark H_{dB} = 20 \cdot \log_{10} \left| 1 + 2\zeta \left(\frac{j\omega}{\omega_0} \right) + \left(\frac{j\omega}{\omega_0} \right)^2 \right|$$

† If $\omega \ll \omega_0$, $|H(j\omega)| \approx 0$

† If $\omega \gg \omega_0$, $|H(j\omega)| \approx 40 \cdot \log_{10} \frac{\omega}{a}$

– asymptote with **40 [dB/decade]**

† When $\omega = \omega_0$, $H_{dB} = 20 \cdot \log_{10} \left| 2\zeta \left(\frac{\omega}{\omega_0} \right) \right|$

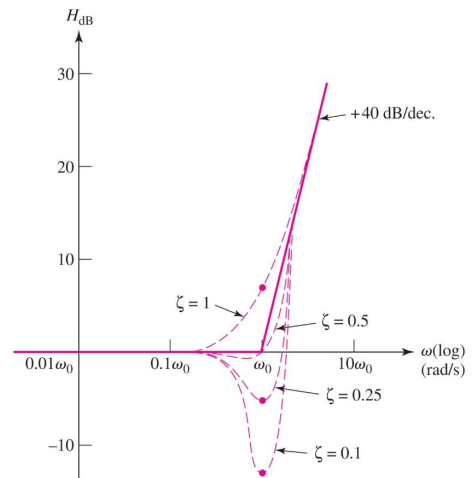

Corrections at corner freq.

(1) $\zeta = 1$, 6 [dB]



(2) $\zeta = 0.5$, 0 [dB]

(3) $\zeta = 0.1$, -14 [dB]


Asymptote 5

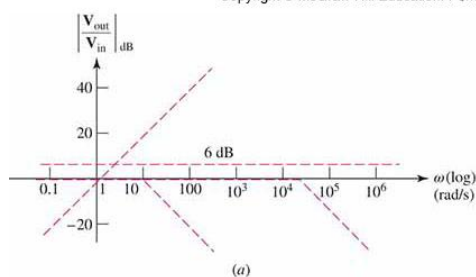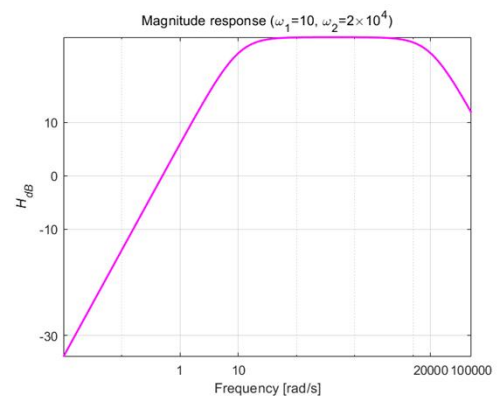• Example 15.3

$$\checkmark H(s) = \frac{V_{out}(s)}{V_{in}(s)} = - \frac{2s}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{20000}\right)}$$



Copyright © McGraw-Hill Education. Permission required for reproduct

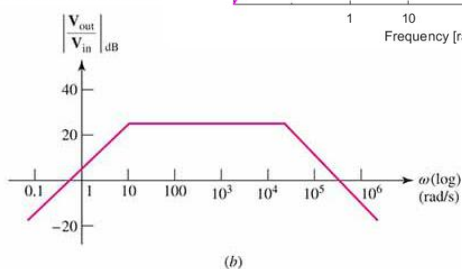


Asymptote 5

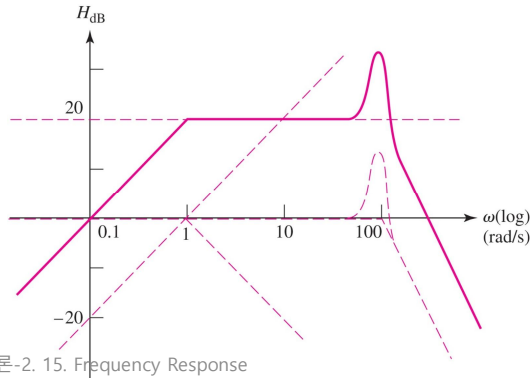
• Example 15.5

$$\checkmark H(s) = \frac{10s}{(1+s)(1+0.002s+0.0001s^2)} = \frac{10s}{\left(1+\frac{s}{\omega_1}\right)\left(1+2\zeta\frac{s}{\omega_2}+\frac{s^2}{\omega_2^2}\right)}$$

† $\zeta = 0.1$, $\omega_1 = 1$, and $\omega_2 = 100$



회로이론-2. 15. Frequency Response

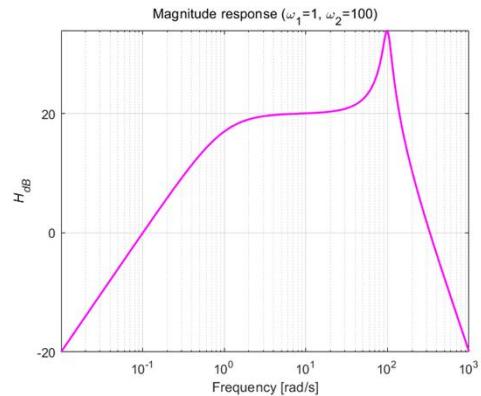

15-9

Parallel Resonance

- The network frequency response can be chosen to reject some frequency components of the forcing function, or to emphasize others.

✓ Turning circuits for radio transmitters/receivers.

- A network is in **resonance** (공진), when voltage and current at input terminals are **in phase**.


✓ Input impedance of the network is **purely resistive**.

- RLC parallel circuit

✓ Admittance seen from the input terminal

$$\checkmark Y = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

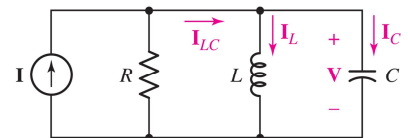✓ Voltage and current are in-phase, if $\omega C - \frac{1}{\omega L} = 0$: $\omega_0 = \frac{1}{\sqrt{LC}}$ (resonant frequency)



회로이론-2. 15. Frequency Response

15-10

Parallel Resonance

- RLC parallel circuit


∨ In s -domain, $Y(s) = \frac{1}{R} + \frac{1}{Ls} + Cs = C \frac{s^2 + \frac{s}{RC} + \frac{1}{LC}}{s}$

∨ $N(s) = s^2 + \frac{1}{RC}s + \frac{1}{LC} = (s + \alpha - j\omega_d)(s + \alpha + j\omega_d)$

† $\alpha = \frac{1}{2RC}$ (exponential damping coefficient, 지수 감쇄계수),

$\omega_0 = \frac{1}{\sqrt{LC}}$ (resonant frequency) and $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ (natural resonant frequency, 고유 공진 주파수)

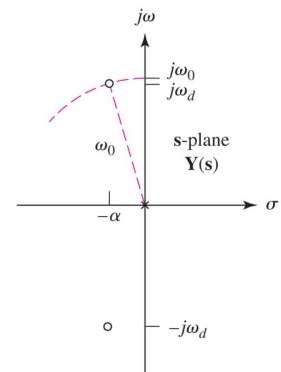† $Y(s)$ has a pole at $s = 0$ and zeros at $s = \alpha \pm j\omega_d$.



회로이론-2. 15. Frequency Response

15-11

Parallel Resonance: Impedance

• Impedance, $Z(s) = \frac{1}{Y(s)} = \frac{s}{C(s + \alpha - j\omega_d)(s + \alpha + j\omega_d)}$

∨ $Z(j\omega) = Z(s)|_{s \leftarrow j\omega} = \frac{j\omega}{C(\alpha + j(\omega - \omega_d))(\alpha + j(\omega + \omega_d))} = \frac{1}{C} \cdot \frac{j\omega}{\omega_0^2 - \omega^2 + j2\alpha\omega}$



∨ $|Z(j\omega)|^2 = \frac{1}{C^2} \cdot \frac{\omega^2}{(\omega_0^2 - \omega^2)^2 + 4\alpha^2\omega^2}$

† $|Z(j\omega)|^2$ attains its maximum at $\omega = \omega_0$

† $|Z(j\omega_0)| = \frac{1}{2\alpha C} = R$

– Impedance has its maximum value at resonance.

Pole-zero pattern of $Z(s)$

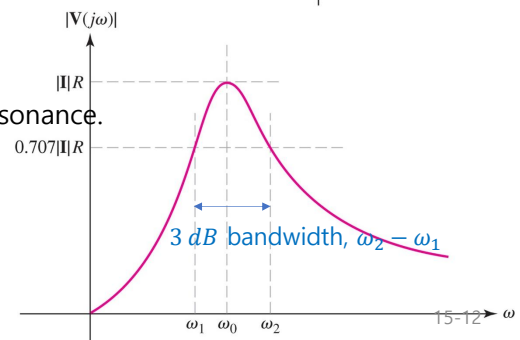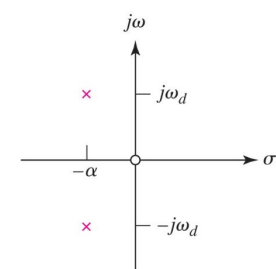

회로이론-2. 15. Frequency Response


Parallel Resonance: Impedance

- In RLC parallel circuit

$$\checkmark I_{L,0} = \frac{V_0}{j\omega_0 L} = \frac{RI}{j} \cdot \frac{\sqrt{LC}}{L} = -jR \sqrt{\frac{C}{L}} I$$

$$\checkmark I_{C,0} = j\omega_0 C V_0 = j \frac{C}{\sqrt{LC}} \cdot RI = jR \sqrt{\frac{C}{L}} I$$
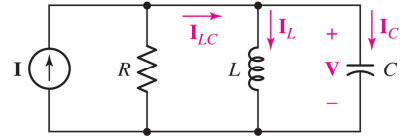
$$\dagger I_{LC,0} = I_{L,0} + I_{C,0} = 0$$



Quality Factor 품질 인자

- 3 dB bandwidth of the magnitude response, $|H(j\omega)|$

$$\checkmark Q = 2\pi \cdot \frac{\text{maximum energy stored}}{\text{total energy lost per period}}$$

$$\checkmark \text{In RLC parallel circuit, } Q = 2\pi \cdot \frac{\max(w_L(t) + w_C(t))}{P_R T}$$

$$\dagger \text{Current source, } i(t) = I_m \cdot \cos \omega_0 t$$

$$\dagger \text{Voltage at resonance, } v(t) = Ri(t) = RI_m \cos \omega_0 t$$

$$\dagger w(t) = w_C(t) + w_L(t) = \frac{1}{2} I_m^2 R^2 C = w_{max}$$

$$- w_C(t) = \frac{1}{2} C v^2 = \frac{1}{2} I_m^2 R^2 C \cdot \cos^2 \omega_0 t, w_L(t) = \frac{1}{2} L i^2 = \frac{1}{2} I_m^2 R^2 C \sin^2 \omega_0 t$$

$$\dagger P_R = \frac{1}{2} I_m^2 R$$

$$\dagger Q_0 = 2\pi \frac{\frac{1}{2} I_m^2 R^2 C}{\frac{1}{2} I_m^2 R} = \omega_0 RC = R \sqrt{\frac{C}{L}}$$

Quality Factor Q_0 & Damping Factor ζ


Copyright © McGraw-Hill Education. Permission required for reproduction or display.

$$\bullet D(s) = s^2 + 2\alpha s + \omega_0^2 = s^2 + 2\zeta\omega_0 s + \omega_0^2 = s^2 + \frac{1}{RC}s + \frac{1}{LC'}$$

$$\vee Y(s) = \frac{C}{s} D(s)$$

$$\vee \zeta = \frac{\alpha}{\omega_0} = \frac{1}{2Q_0}$$
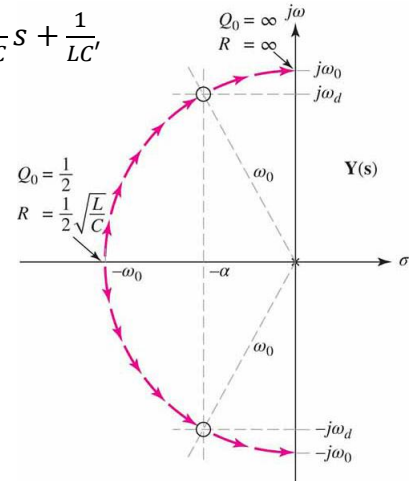
$$\vee \omega_d = \sqrt{\omega_0^2 - \alpha^2} = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2}$$



Constant L and C : constant ω_0

회로이론-2. 15. Frequency Response

15-15

3-dB Bandwidth

- 3 dB bandwidth, $B = \omega_1 - \omega_2$

$$\vee \omega_{1,2} \dots \text{half-power frequency: } |V(j\omega_{1,2})|^2 = \frac{1}{2} |V(j\omega_0)|^2$$

\vee In RLC parallel circuit,


$$\dagger Y(j\omega) = \frac{1}{R} \left(1 + jQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right)$$

$$\dagger Y(j\omega_0) = \frac{1}{R} \text{ and } |Y(j\omega_{1,2})| = \frac{\sqrt{2}}{R}$$

– It happens only if the imaginary part is ± 1 .

$$- Q_0 \left(\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2} \right) = 1 \text{ or } Q_0 \left(\frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1} \right) = -1 \Rightarrow \omega_{1,2} = \omega_0 \left(\sqrt{1 + \left(\frac{1}{2Q_0} \right)^2} \mp \frac{1}{2Q_0} \right)$$
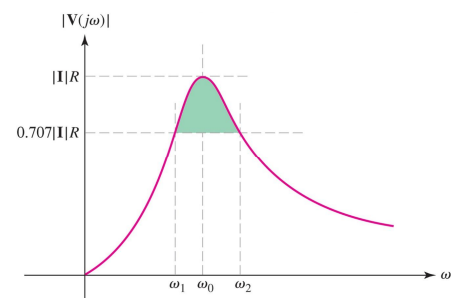
$$- B = \omega_2 - \omega_1 = \frac{\omega_0}{Q_0}$$



회로이론-2. 15. Frequency Response

15-16

High-Q Circuit

- High $Q_0 \Rightarrow$ Narrow B/W and high frequency selectivity
- When $Q_0 > 5$,

$$\vee \alpha = \frac{\omega_0}{2Q_0} = \frac{1}{2}B \text{ and } \omega_d = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2} \approx \omega_0$$

$$\vee \text{Zeros of } Y(s), s_{1,2} = -\alpha \pm j\omega_d \approx -\frac{1}{2}B \pm j\omega_0$$

$$\vee \omega_{1,2} = \omega_0 \left(\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} \mp \frac{1}{2Q_0} \right) \approx \omega_0 \left(1 \mp \frac{1}{2Q_0} \right) = \omega_0 \mp \frac{1}{2}B$$

$$\dagger |\omega_1 - \omega_0| = |\omega_2 - \omega_0| = \frac{B}{2} \dots \text{symmetrical half-power frequency around } \omega_0$$

$$\dagger \omega_0 \approx \frac{1}{2}(\omega_1 + \omega_2) \dots \text{arithmetic mean}$$

Series RLC Resonance

- RLC series circuit with $v_s(t) = \cos \omega t$

$$\vee Ri + L \frac{di}{dt} + \frac{1}{C} \int^t i(\tau) d\tau = v_s(t), \left(R + Ls + \frac{1}{Cs} \right) I(s) = V_s(s)$$

$$\vee Z(s) = \frac{V_s(s)}{I(s)} = R + Ls + \frac{1}{Cs} \text{ or } Z(j\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j \left(\omega L - \frac{1}{\omega C} \right)$$


$$\dagger \text{Resonant frequency, } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\dagger \text{Series current at resonance, } i(t) = \frac{1}{R} \cos \omega_0 t$$

$$- w_C(t) = \frac{1}{2} C v_C^2(t) = \frac{L}{2R^2} \sin^2 \omega_0 t, w_L(t) = \frac{1}{2} L i^2(t) = \frac{L}{2R^2} \cos^2 \omega_0 t$$

$$- w(t) = w_C(t) + w_L(t) = \frac{L}{2R^2}$$
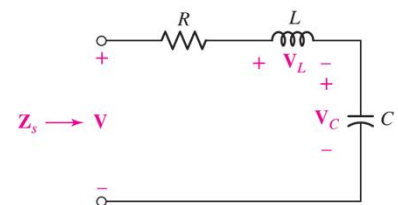
$$- P_R T = \frac{1}{2} I_m^2 R \cdot T = \frac{1}{2R} \cdot \frac{1}{f_0}$$



Series RLC Resonance

$$\vee Q_0 = 2\pi \frac{L}{2R^2} \cdot 2f_0 R = \omega_0 \frac{L}{R}$$

$$\dagger Q_0 = \omega_0 RC \text{ in RLC parallel circuit}$$

$$\dagger \text{ Half-power frequency, } \omega_{1,2} = \omega_0 \left(\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} \mp \frac{1}{2Q_0} \right)$$

$$\dagger B = \omega_2 - \omega_1 = \frac{\omega_0}{Q_0}$$

\vee At resonance,

$$\dagger V_L(j\omega_0) = j\omega_0 L \cdot \frac{\mathbf{V}}{R} = jQ_0 \mathbf{V}$$

$$\dagger V_C(j\omega_0) = \frac{1}{j\omega_0 C} \cdot \frac{\mathbf{V}}{R} = -jQ_0 \mathbf{V}$$

$$\dagger V_C(j\omega_0) + V_L(j\omega_0) = 0$$

$$- I_C(j\omega_0) + I_L(j\omega_0) = 0, \text{ in RLC parallel circuit}$$

Realistic Circuit Model

- Circuit with physical inductor & capacitor

\vee Resonance, when $\text{Im}\{Y(j\omega)\} = 0$

$$\dagger Y(j\omega) = \frac{1}{R_1 + j\omega L} + j\omega C + \frac{1}{R_2}$$


$$- Y(j\omega) = \frac{R_1 - j\omega L}{R_1^2 + \omega^2 L^2} + j\omega C + \frac{1}{R_2} = \left(\frac{1}{R_2} + \frac{R_1}{R_1^2 + \omega^2 L^2} \right) + j \left(\omega C - \frac{\omega L}{R_1^2 + \omega^2 L^2} \right)$$

$$\dagger \text{Im}\{Y(j\omega)\} = 0 \Rightarrow C = \frac{L}{R_1^2 + \omega^2 L^2} \text{ or } \omega_0 = \sqrt{\frac{1}{LC} - \left(\frac{R_1}{L}\right)^2}$$

$$- \omega_0 < \sqrt{\frac{1}{LC}}$$

– Maximum magnitude of input impedance does not occur at ω_0 .

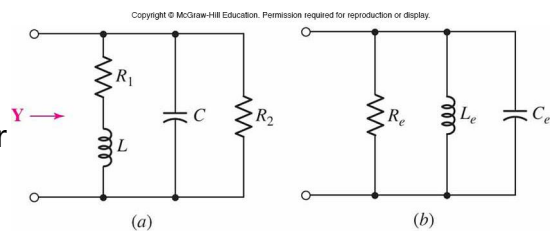– Practical RLC circuit can be modeled with an ideal RLC circuit over a narrow frequency band (see Figure, part (b)).



Realistic Circuit Model


- **Example 15.9** $R_1 = 2 [\Omega]$, $L = 1 [H]$, $C = 125 [mF]$, and $R_2 = 3 [\Omega]$

$$\vee Y(j\omega) = \frac{1}{R_1 + j\omega L} + j\omega C + \frac{1}{R_2} \text{ and } Z(j\omega) = \frac{1}{Y(j\omega)}$$

$$\vee \omega_0 = \sqrt{\frac{1}{LC} - \left(\frac{R_1}{L}\right)^2} = 2 [\text{rad/s}]$$

$$\dagger Y(j\omega_0) = \frac{1}{2 + j2} + j2 \cdot \frac{1}{8} + \frac{1}{3} = \frac{7}{12} [S] \text{ and } Z(j\omega_0) = \frac{12}{7} [\Omega]$$

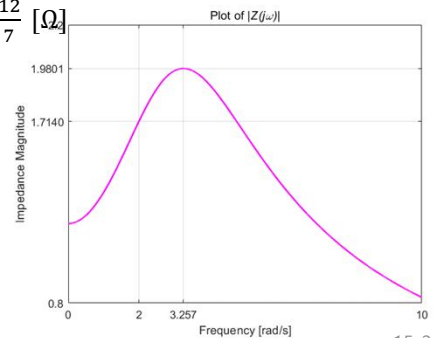
† Maximum impedance magnitude at $\omega = 3.257$




회로이론-2. 15. Frequency Response

15-21


Basic Filter Design

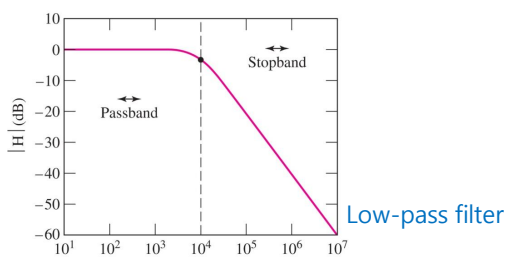


Low-pass filter

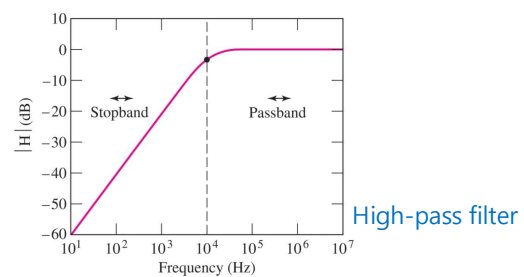

High-pass filter

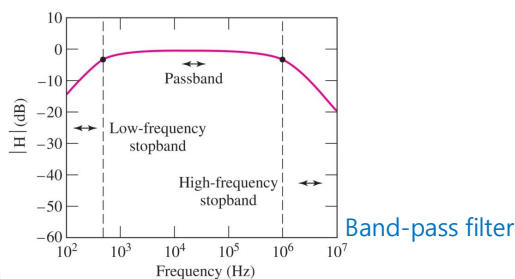

Band-pass filter

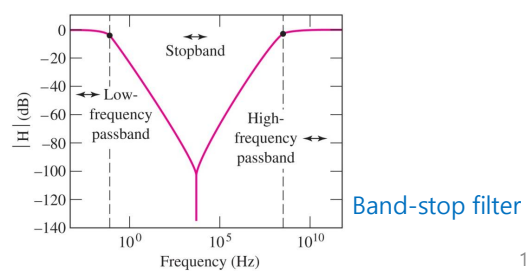

Band-stop filter

회로이론 - Frequency Response

15-22

Low-pass Filter



- Low-pass filter, $H(s) = \frac{1}{1+RCs}$

✓ Corner frequency at $\omega = \frac{1}{RC}$

† At $\omega = 0$ (DC), capacitor acts like an open-circuit: $V_{out}(j\omega) = V_{in}(j\omega)$

† As $\omega \rightarrow \infty$, capacitor acts like a short-circuit: $Z_C = \frac{1}{j\omega C} \rightarrow 0$, $V_{out}(j\omega) = 0$

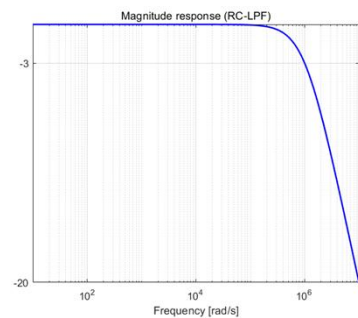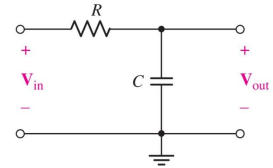✓ $R = 100 [\Omega]$ and $C = 2 [nF]$: $\omega = 10^6 [rad/s]$



회로이론-2. 15. Frequency Response

15-23

High-pass Filter

- High-pass filter, $H(s) = \frac{RCs}{1+RCs}$



✓ Zero at $s = 0$ and pole at $s = -\frac{1}{RC}$

✓ Corner frequency at $\omega_c = \frac{1}{RC}$

† At $\omega = 0$ (DC), capacitor acts like an open-circuit: $V_{out}(j\omega) = 0$

† As $\omega \rightarrow \infty$, capacitor acts like a short-circuit: $V_{out}(j\omega) = V_{in}(j\omega)$

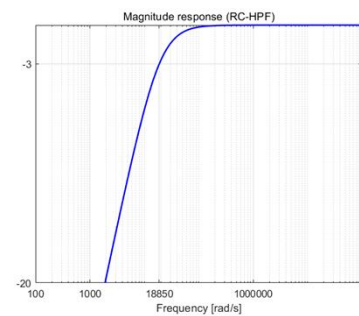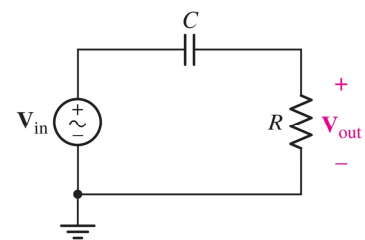
✓ $R = 4.7 [k\Omega]$ and $C = 11.29 [nF]$: $\omega_c = 18.85 \times 10^3 [rad/s]$



회로이론-2. 15. Frequency Response

15-24

Band-pass Filter

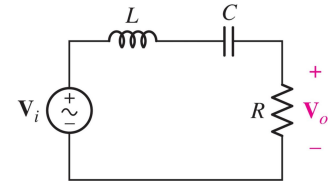

$$\bullet H(s) = \frac{V_o(s)}{V_i(s)} = \frac{RCs}{LCs^2 + RCs + 1} \text{ or } H(j\omega) = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC}$$

✓ When $\omega = 0$, $V_o(j\omega) = 0$ and so is when $\omega \rightarrow \infty$.

✓ Center frequency at $\omega = \frac{1}{\sqrt{LC}}$

✓ At half-power frequencies, $|H(j\omega_c)| = \frac{\omega_c RC}{\sqrt{(1 - \omega_c^2 LC)^2 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$

$$\dagger (1 - \omega_c^2 LC)^2 = \omega_c^2 R^2 C^2 \Rightarrow 1 - \omega_c^2 LC = \pm \omega_c RC$$

– leading to two solutions $\omega_{H,L}$

$$- 1 - \omega_L^2 LC = \omega_L RC \text{ and } 1 - \omega_H^2 LC = -\omega_H RC$$

$$\dagger B = \omega_H - \omega_L = \frac{R}{L}$$

Band-pass Filter

- Example 15.13 BPF with $B = 1$ [MHz] and $f_H = 1.1$ [MHz]

$$\dagger f_L = f_H - B = 100 \text{ [kHz]},$$

$$\dagger \omega_L = 2\pi f_L = 628.3 \times 10^3 \text{ [rad/s]} \text{ and } \omega_H = 2\pi f_H = 6.912 \times 10^6 \text{ [rad/s]}$$

$$\dagger B = 2\pi \times 10^6 \text{ [rad/s]}$$

$$\vee 1 - \omega_H^2 LC = -\omega_H RC \Rightarrow \omega_H^2 - B\omega_H = \frac{1}{LC} \left(B = \frac{R}{L} \right)$$

$$\dagger \frac{1}{LC} = 4.3464 \times 10^{12}$$

✓ Choose $L = 50$ [mH]. Then, $R = BL = \pi \times 10^5$ [Ω] and $C = 4.602 \times 10^{-12}$ [F]

