

Chapter 3. Voltage & Current laws

1. Network topology: Nodes, paths, loops, and branches
2. KCL / KVL
3. Single-loop / -node-pair circuits
4. Series & parallel connections
5. Voltage & current division

회로이론-1. 2. Voltage and Current laws

1

Network topology: Nodes, paths, loops, branches

- Terminologies based on graph theory


- ✓ Every circuit element can be represented by a branch with two terminals.
- ✓ **Node (마디)**: A point at which two or more circuit elements have a common connection.
 - ✓ 두 개 이상의 회로소자는 node로 연결된다.
 - ✓ Every circuit element has a pair of nodes at each of its ends.
- ✓ **Branch (가지)**: A single path in a network, composed of one circuit element and nodes at each end.
- ✓ A path is a sequence of nodes/branches.
- ✓ A **loop** is a closed path
 - † 한 node에서 시작하여 node 반복 없이 시작 node로 다시 돌아오는 폐경로.

회로이론-1. 3. Voltage and Current laws

3-2

Nodes, paths, loops, branches

- Example

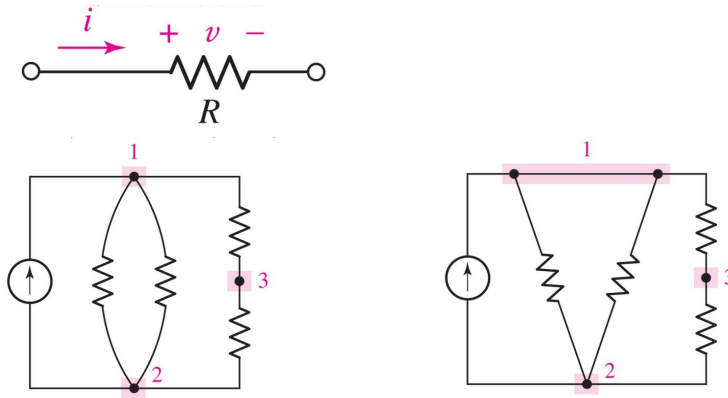


회로이론-1. 3. Voltage and Current laws

3-3

KCL, Kirchhoff's Current Law

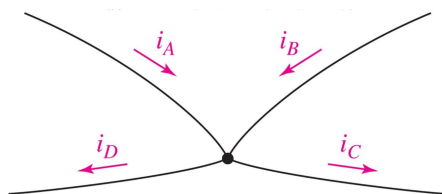- KCL: Algebraic sum of branch currents entering any node is zero.



$$i_A + i_B + (-i_C) + (-i_D) = 0$$


$$i_A + i_B = i_C + i_D$$

회로이론-1. 3. Voltage and Current laws

3-4


KCL

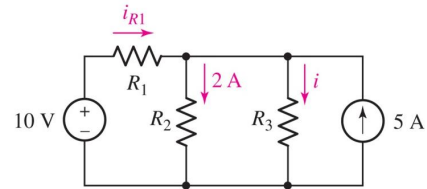- **Example 3.1** Find the current through resistor R_3 , if the voltage source supplies a current of 3 [A].




Copyright © McGraw-Hill Education. Permission required for reproduction or display.

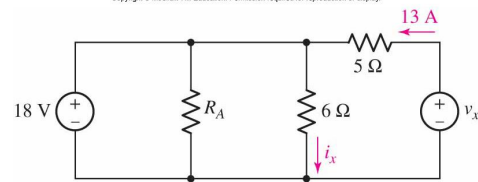- **Practice 3.1** Find R_A , when $i_x = 3[A]$ and the voltage source delivers 8[A] current.



KVL, Kirchhoff's Voltage Law

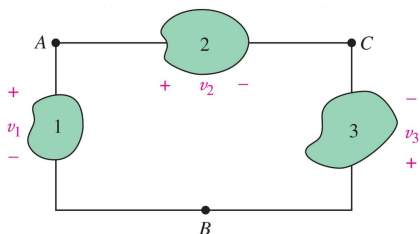- KVL: Algebraic sum of branch voltages around any closed path is zero.




Starting from the node-A, add-up branch voltages while checking the voltage polarities:

$$v_2 + (-v_3) + (-v_1) = 0$$


$$v_2 = v_1 + v_3$$

KVL

- Example 3.2 Find v_x and i_x .

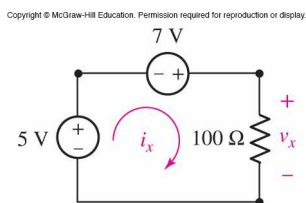

- Practice 3.2 Find v_x and i_x .

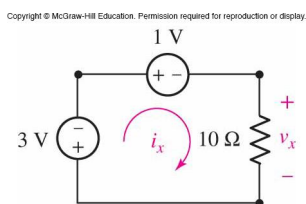


회로이론-1. 3. Voltage and Current laws


3-7

KVL

- Example 3.3 Find v_{R2} and v_x .

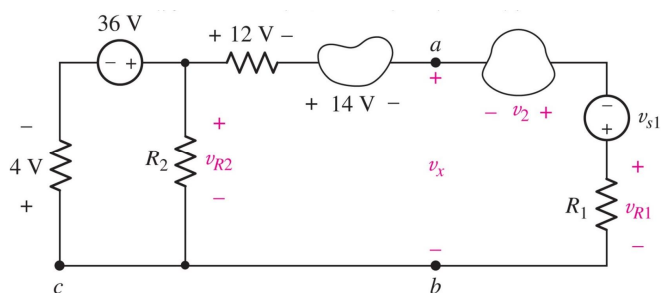

- Example 3.4 Find v_x and i_x .

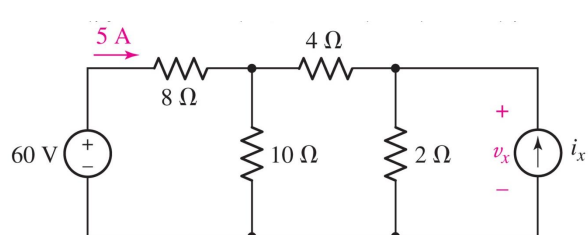

회로이론-1. 3. Voltage and Current laws


3-8

Series Connection 직렬 연결

- All elements in a circuit that carry the same current are said to be connected in **series**.

✓ 직렬 연결된 소자는 **동일한 전류** 값을 공유한다.

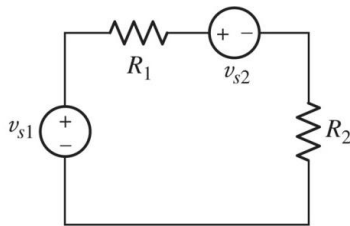✓ 하나의 node를 두 개의 branch(혹은 회로소자) 만이 공유할 때 두 소자는 직렬연결 된다.



회로이론-1. 3. Voltage and Current laws


3-9

Parallel Connection 병렬 연결

- Elements in a circuit having a **common voltage** across them are said to be connected in **parallel**.

✓ 병렬 연결된 소자는 **동일한 전압** 값을 공유한다.

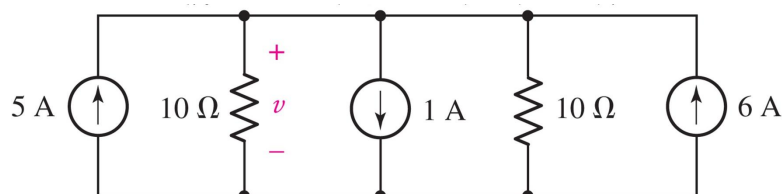✓ 한 쌍의 node를 공유하는 두 개 이상의 branch는 병렬연결 된다.



회로이론-1. 3. Voltage and Current laws

3-10

감전 사고

Physiological reactions to current levels in humans

Physiological reaction	Current
Barely perceptible	3 ~ 5 [mA]
Extreme pain	30 ~ 50 [mA]
Muscle paralysis	50 ~ 70 [mA]
Heart stoppage	500 [mA]

감전에 의한 인체의 위험도

1. 전류의 크기
2. 통전 시간
3. 통전 경로
4. 전원의 종류



postastock.com - 46182187

회로이론-1. 3. Voltage and Current laws


- 감전의 위험도 \propto (접촉전압의 크기) \times (감전시간)
- 허용 접촉 전압
 - ✓ 일반 환경: 50 [V]
 - ✓ 젖어 있는 상태: 25 [V]
 - ✓ 물속: 2.5[V] 이하
- 평균 인체 저항: 500 ~ 5,000 [Ω]

3-11

Single-loop circuit

✓ A circuit where all circuit elements (or branches) are series-connected.

- Example 3.5 Compute powers.

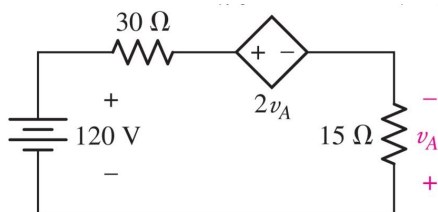


회로이론-1. 3. Voltage and Current laws

3-12

Single-node-pair circuit

✓ A circuit where all branches share a pair of nodes.

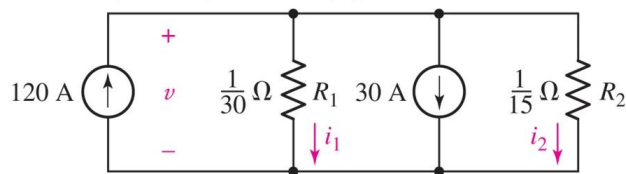- **Example 3.6** Compute all circuit variables.




회로이론-1. 3. Voltage and Current laws


3-13

Single-node-pair circuit

- **Example 3.7** Find the voltage, v .

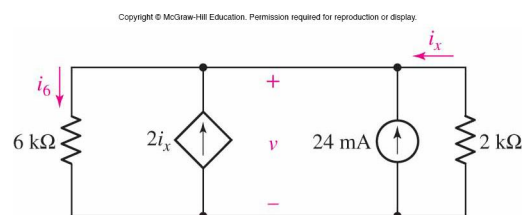

- **Practice 3.8** Find i_A .

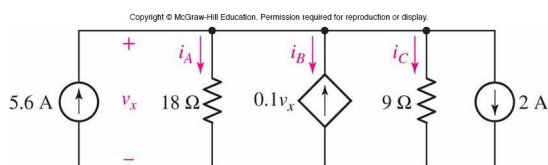


회로이론-1. 3. Voltage and Current laws


3-14

Series & parallel connection of sources

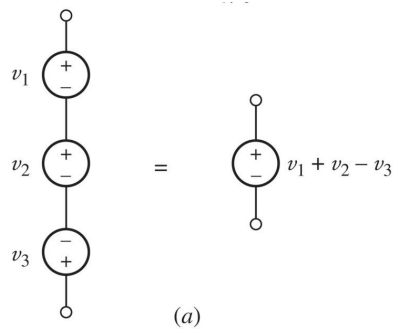- Voltage sources connected in series can be combined into an equivalent voltage source:



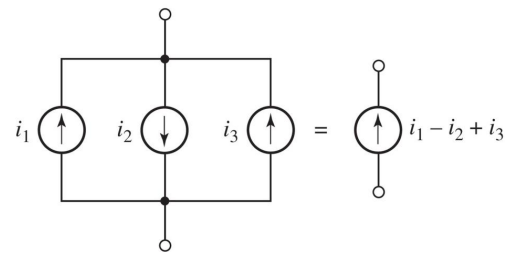- Current sources connected in parallel can be combined into an equivalent current source:




회로이론-1. 3. Voltage and Current laws

3-15

Impossible circuits

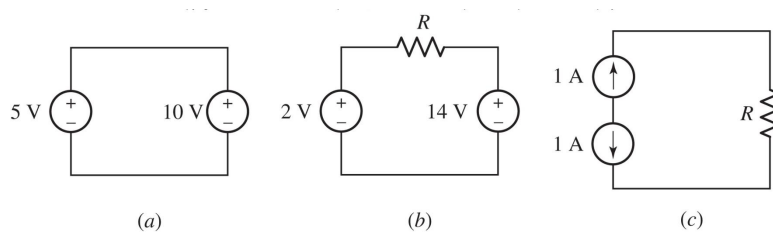- Parallel-connected voltage sources / series-connected current sources




- ❖ 어떤 전자기기의 전원부는 1.5[V] battery 4개가 병렬연결 되도록 구성되어 있다. 찾아보니, 새 건전지가 2개밖에 없어서, 나머지 2개는 사용하던 건전지를 사용하였다. 어떤 문제점이 있을까?

회로이론-1. 3. Voltage and Current laws

3-16

Series connection of resistors

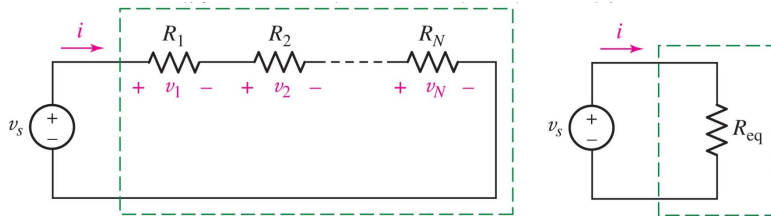


$$\text{KVL: } v_1 + v_2 + \dots + v_N = v_s, (R_1 + R_2 + \dots + R_N)i = R_{eq}i = v_s$$

- 등가 저항 (equivalent resistance)
 - ✓ Terminal a-b에서 바라본 등가저항
 - ✓ 동일한 전류-전압 특성


Series connection of resistors

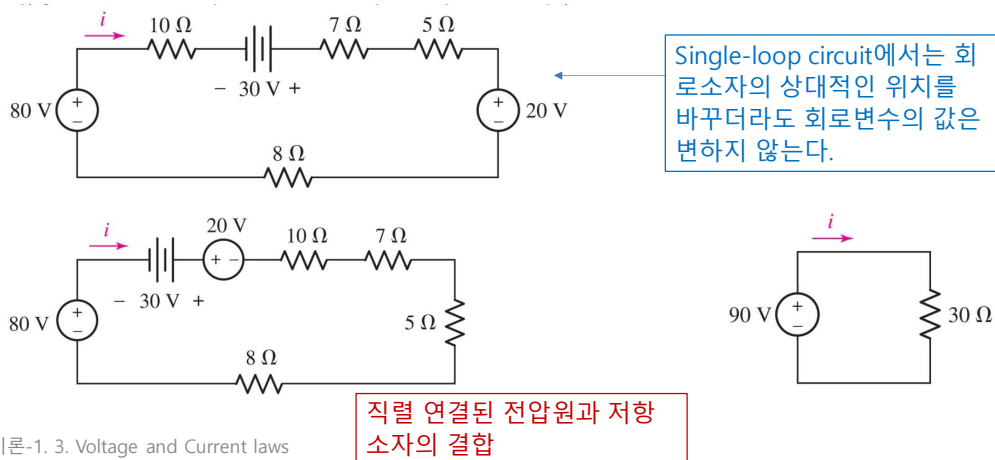- Example 3.11 Find i and the power supplied by the 80 [V] voltage source.




Series connection of resistors

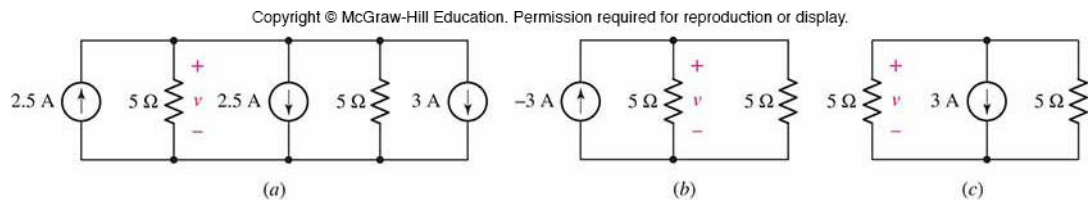- **Example 3.12** Find the power supplied by the voltage source.



Parallel connection of resistors

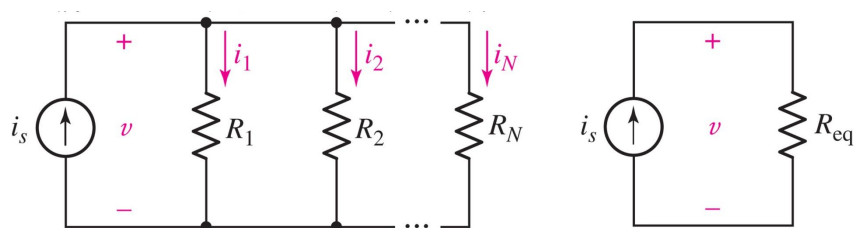


$$\text{KCL: } i_1 + i_2 + \cdots + i_N = i_s, \left(\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N} \right) v = \frac{1}{R_{eq}} v = i_s$$

- Two resistors in parallel

$$v \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}, R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Voltage division

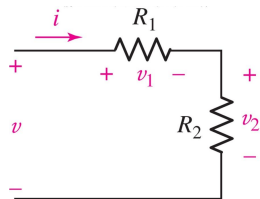
- Resistors in series "share" the applied voltage.



$$v_1 = R_1 i, \quad v_2 = R_2 i, \quad v_1 + v_2 = v, \quad \text{and} \quad i = \frac{v}{R_1 + R_2}$$

Thus, $v_1 = \frac{R_1}{R_1 + R_2} v$ and $v_2 = \frac{R_2}{R_1 + R_2} v$

- Example 3.13** Find v_x .

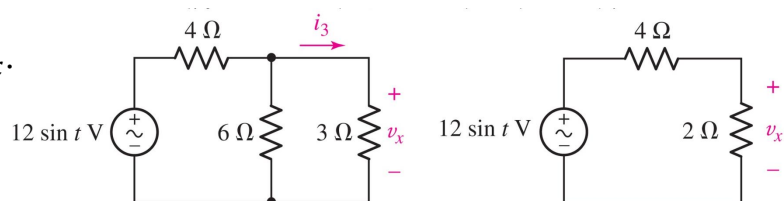


회로이론-1. 3. Voltage and Current laws

3-21

Current division

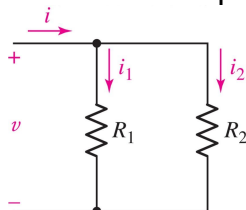
- Resistors in parallel "share" current through them.



$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}, \quad i_1 + i_2 = i, \quad \text{and} \quad v = (R_1 \parallel R_2) i = \frac{R_1 R_2}{R_1 + R_2} i$$

Thus, $i_1 = \frac{R_2}{R_1 + R_2} i$ and $i_2 = \frac{R_1}{R_1 + R_2} i$

- Practice 3.14** Find v_3 .

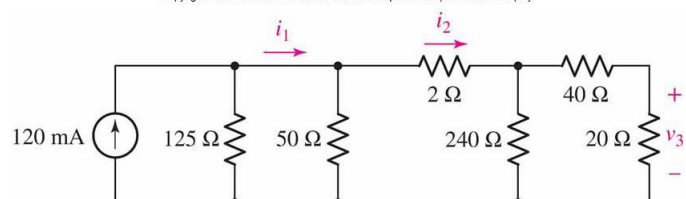


Copyright © McGraw-Hill Education. Permission required for reproduction or display.

회로이론-1. 3. Voltage and Current laws

3-22

Wheatstone bridge

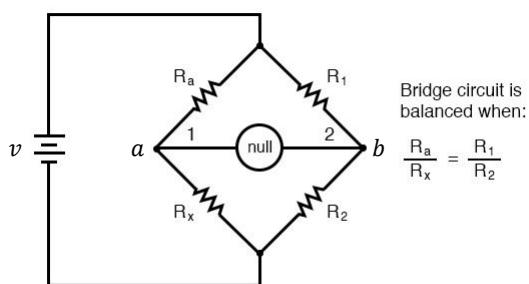- How to measure the resistance of medium range: $1 \sim 10^6 [\Omega]$.
 - ✓ 4 resistors, R_1 , R_2 , R_a , known, while R_x unknown.
 - ✓ dc voltage source and current detector.



When $i_{ab} = 0$,

(1) $i_a = i_x$ and $i_1 = i_2$

(2) $R_a i_a = R_1 i_1$ and $R_x i_x = R_2 i_2$

(3) $\frac{R_x}{R_2} = \frac{i_2}{i_x} = \frac{i_1}{i_a} = \frac{R_a}{R_1}$

$$R_x = \frac{R_2}{R_1} R_a$$


회로이론-1. 3. Voltage and Current laws

3-23


Ground, 접지

- A point with zero electrical potential.
 - ✓ Reference to all other voltages

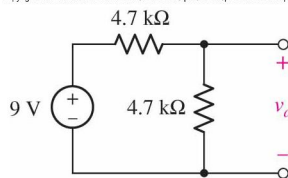
Copyright © McGraw-Hill Education. Permission required for reproduction or display.



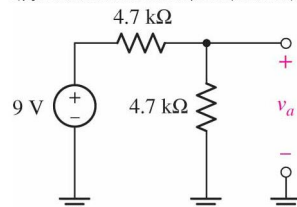Copyright © McGraw-Hill Education. Permission required for reproduction or display.



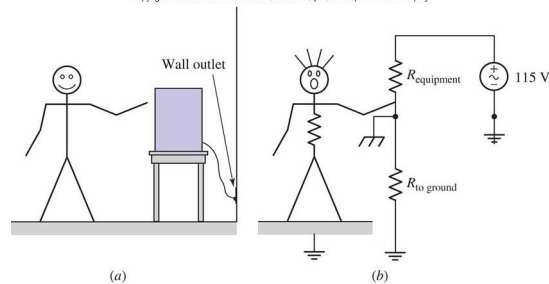Copyright © McGraw-Hill Education. Permission required for reproduction or display.



회로이론-1. 3. Voltage and Current laws

3-24