

Chapter 11. AC Circuit: Power Analysis

1. Instantaneous Power
2. Average power and Effective Value
3. Apparent power, Power factor, and Complex power
4. Power factor correction

회로이론-2. 11. AC Power Analysis

11-1

Instantaneous Power 순시 전력

- $p(t) = v(t)i(t)$

- ✓ $p(t) = i^2(t)R = \frac{1}{R}v^2(t)$, in a resistor

- ✓ $p(t) = Li(t)\frac{di(t)}{dt} = \frac{1}{L}v(t)\int^t v(\tau)d\tau$, in a conductor or



- ✓ $p(t) = Cv(t)\frac{dv(t)}{dt} = \frac{1}{C}i(t)\int^t i(\tau)d\tau$, in a capacitor

- Given $i(t) = \frac{V_0}{R}\left(1 - e^{-\frac{Rt}{L}}\right)u(t)$

- ✓ **Power supplied:** $p(t) = v_s(t)i(t) = \frac{V_0^2}{R}\left(1 - e^{-\frac{Rt}{L}}\right)u(t) = p_R(t) + p_L(t)$, where

- † $p_R(t) = i^2(t)R = \frac{V_0^2}{R}\left(1 - e^{-\frac{Rt}{L}}\right)^2 u(t)$

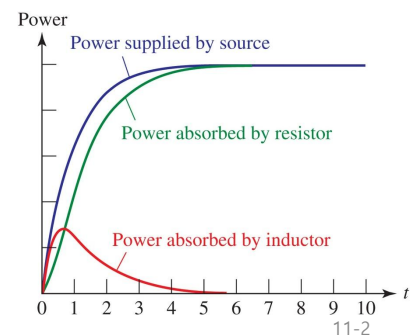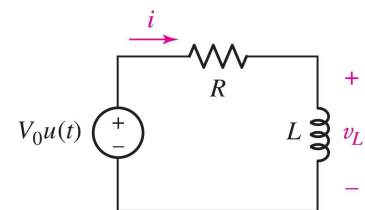- † $p_L(t) = v_L(t)i(t) = V_0 e^{-\frac{Rt}{L}} \cdot \frac{V_0}{R}\left(1 - e^{-\frac{Rt}{L}}\right)u(t)$



회로이론-2. 11. AC Power Analysis

11-2

Power from Sinusoidal Source

- RL series circuit with $v_s(t) = V_m \cos \omega t$:

$$\vee i(t) = I_m \cos(\omega t + \phi)$$

$$\text{where } I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \text{ and } \phi = -\tan^{-1} \frac{\omega L}{R}$$

- ∨ Instantaneous power,

$$\dagger p(t) = v_s(t)i(t) = V_m I_m \cos \omega t \cdot \cos(\omega t + \phi) = \frac{1}{2} V_m I_m (\cos \phi + \cos(2\omega t + \phi))$$

† Constant term + double frequency term

Average Power 평균 전력

- Average power over an interval, $[t_1, t_2]$

$$\vee P_{avg} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$

- Periodic $p(t)$ with period T


$$\vee P_{avg} = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$

- When $v(t) = V_m \cdot \cos(\omega t + \theta)$ and $i(t) = I_m \cdot \cos(\omega t + \phi)$ with $\omega = \pi/6$

$$\vee p(t) = v(t)i(t) = \frac{1}{2} V_m I_m (\cos(\theta - \phi) + \cos(2\omega t + \theta + \phi)).$$

$$\vee P_{avg} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$
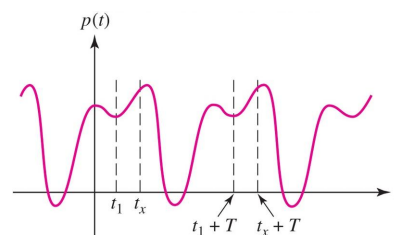
$$\vee P_{avg} = \frac{1}{2} \text{Re}\{\mathbf{VI}^*\}$$



Average Power 평균 전력

- **Example 11.2** Voltage $v(t) = 4 \cos \pi t/6$ across an impedance $\mathbf{Z} = 2 \angle 60^\circ$

$$\checkmark \mathbf{V} = 4 \angle 0^\circ$$


$$\checkmark \mathbf{I} = 2 \angle -60^\circ$$

$$\checkmark P_{avg} = \frac{1}{2} 4 \cdot 2 \cdot \cos 60^\circ = 2 \text{ [W]}$$

$$\checkmark i(t) = 2 \cos\left(\frac{\pi t}{6} - 60^\circ\right)$$

$$\checkmark p(t) = 8 \cos \frac{\pi t}{6} \cdot 2 \cos\left(\frac{\pi t}{6} - 60^\circ\right)$$
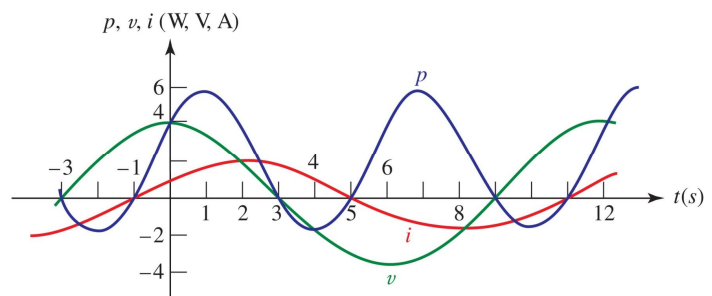
$$= 2 + 4 \cos\left(\frac{\pi t}{3} - 60^\circ\right)$$



회로이론-2. 11. AC Power Analysis

11-5

Average Power in Passive Elements

- Resistor, $\theta = \phi$ (in-phase)

$$\checkmark P_{avg}(t) = \frac{1}{2} \frac{V_m}{R}$$

- Inductor and capacitor, $\theta - \phi = \pm 90^\circ$

$$\checkmark P_{avg}(t) = 0$$

† Average power absorbed by a purely reactive element(s) is zero, due to 90° phase difference between voltage and current.

회로이론-2. 11. AC Power Analysis

11-6

Average Power: Example

- **Example 11.3** Impedance $\mathbf{Z}_L = 8 - j11 \text{ } [\Omega]$ with current $\mathbf{I} = 5\angle 20^\circ \text{ } [A]$

$$\vee \mathbf{V} = \mathbf{Z}_L \mathbf{I} = (13.6015\angle -53.9726^\circ) \cdot 5\angle 20^\circ = 68.0074\angle -33.9726^\circ \text{ } [V]$$

$$\dagger P_{avg} = \frac{1}{2} 68.0074 \cdot 5 \cdot \cos(-33.9726^\circ - 20^\circ) = 100 \text{ } [W]$$

$$\vee P_{avg} = \frac{1}{2} I_m^2 R = \frac{1}{2} \cdot 5^2 \cdot 8 = 100 \text{ } [W]$$

† The reactance part of impedance does not observe average power.

$$\vee P_{avg} = \frac{1}{2} \text{Re}\{\mathbf{VI}^*\} = \frac{1}{2} \text{Re}\{(68.0074\angle -33.9726^\circ) \cdot 5\angle 20^\circ\}$$

Average Power: Example

- **Example 11.4**

∨ Note that average power absorbed by two reactive element is zero.

$$\vee j2\mathbf{I}_1 + 2(\mathbf{I}_1 - \mathbf{I}_2) = 20, \quad -j2\mathbf{I}_2 + 10 = 2(\mathbf{I}_1 - \mathbf{I}_2)$$

$$\dagger \mathbf{I}_1 = 5 - j10 = 11.18\angle -63.43^\circ \text{ and } \mathbf{I}_2 = 5 - j5 = 5\sqrt{2}\angle -45^\circ$$

$$\dagger \mathbf{I}_1 - \mathbf{I}_2 = -j5 = 5\angle -90^\circ$$

$$\vee \text{Avg. power in resistor: } P_R = \frac{1}{2} I_m^2 R = \frac{1}{2} \cdot 5^2 \cdot 2 = 25 \text{ } [W]$$

∨ In the **left voltage source**,

$$\dagger \mathbf{V}_L = 20\angle 0^\circ \text{ and } \mathbf{I}_1 = 11.18\angle -63.43^\circ \Rightarrow P_L = \frac{1}{2} 20 \cdot 11.18 \cdot \cos 63.43^\circ = 50 \text{ } [W]$$

∨ In the **right voltage source**,

$$\dagger \mathbf{V}_R = 10\angle 0^\circ \text{ and } \mathbf{I}_2 = 5\sqrt{2}\angle -45^\circ \Rightarrow P_R = \frac{1}{2} 10 \cdot 5\sqrt{2} \cdot \cos 45^\circ = 25 \text{ } [W]$$


Maximum Power Transfer

- A Thevenin equivalent circuit connected to load impedance:

$$\checkmark \mathbf{I}_L = \frac{\mathbf{V}_{th}}{\mathbf{Z}_{th} + \mathbf{Z}_L} = \frac{\mathbf{V}_{th}}{R_{th} + R_L + j(X_{th} + X_L)}$$

$$\text{where } \mathbf{V}_{th} = R_{th} + jX_{th}, \mathbf{Z}_L = R_L + jX_L$$

$$|\mathbf{I}_L| = \frac{|\mathbf{V}_{th}|}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} \text{ and } \angle \mathbf{I}_L = \angle \mathbf{V}_{th} - \tan^{-1} \left(\frac{X_{th} + X_L}{R_{th} + R_L} \right)$$

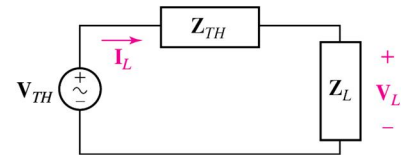

$$\checkmark \mathbf{V}_L = \frac{\mathbf{Z}_L}{\mathbf{Z}_{th} + \mathbf{Z}_L} \mathbf{V}_{th} = \frac{R_L + jX_L}{R_{th} + R_L + j(X_{th} + X_L)} \mathbf{V}_{th}$$

$$\text{where } |\mathbf{V}_L| = \frac{|\mathbf{V}_{th}| \sqrt{R_L^2 + X_L^2}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} \text{ and } \angle \mathbf{V}_L = \angle \mathbf{V}_{th} + \tan^{-1} \frac{X_L}{R_L} - \tan^{-1} \left(\frac{X_{th} + X_L}{R_{th} + R_L} \right)$$

$$\checkmark P_L = \frac{1}{2} |\mathbf{V}_{th}|^2 \frac{\sqrt{R_L^2 + X_L^2}}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \cos \left(\tan^{-1} \frac{X_L}{R_L} \right) = \frac{1}{2} |\mathbf{V}_{th}|^2 \frac{R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$


$$\frac{\partial P}{\partial R_L} = 0 \text{ and } \frac{\partial P}{\partial X_L} = 0 \Rightarrow R_L = R_{th} \text{ and } X_L = -X_{th} \text{ or } \mathbf{Z}_L = \mathbf{Z}_{th}^*$$

Maximum Power Transfer

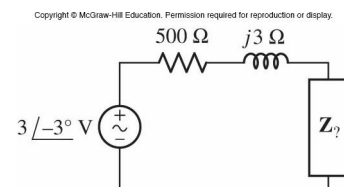- Example 11.7 $v_s(t) = 3 \cdot \cos(100t - 3^\circ)$

✓ Series connection to an impedance, \mathbf{Z}_L

✓ For maximum power transfer to load, $\mathbf{Z}_L = \mathbf{Z}_{th}^* = 500 - j3$



Effective Value 실효값

- Consider the voltage supplied to a household.
 - 220[V]/60[Hz], compared 120/60 in America, 220/50 in Europe, 100/60 or 100/50 in Japan.
 - $v(t) = 220\sqrt{2} \cdot \cos(2\pi 60t)$ with $V_m = 220\sqrt{2}$ [V]


- Effective value of a periodic signal

- When $i(t)$ is periodic, its **effective value** is equal to the value of the direct current (dc) which delivers the same average power to the resistor as does the periodic current to a R [Ω] resistor.

- In DC, $P = I_{eff}^2 R$

- In periodic current,
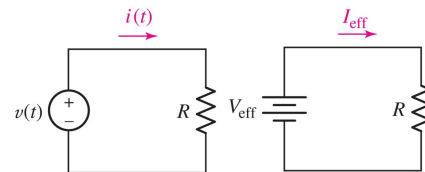
$$P_{avg} = \frac{1}{T} \int_0^T i^2(t) R dt = \frac{R}{T} \int_0^T i^2(t) dt$$



회로이론-2. 11. AC Power Analysis

11-11

Effective Value

- $I_{eff}^2 R = \frac{1}{T} \int_0^T i^2(t) dt$

- $I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$... rms(root mean squared) value

- Sinusoidal current**

- $i(t) = I_m \cos(\omega t + \phi)$

- $I_{eff} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt} = \frac{1}{\sqrt{2}} I_m$

- $P_{avg} = \frac{1}{2} I_m^2 R = I_{eff}^2 R = \frac{V_{eff}^2}{R}$

- $P_{avg} = V_{eff} I_{eff} \cos(\theta - \phi)$

In practice, the effective value is usually used in the fields of power transmission or distribution and of rotating machinery; in the areas of electronics and communications, the amplitude is more often used.

회로이론-2. 11. AC Power Analysis

11-12

Apparent Power 피상전력 & Power Factor 역률

- When $v(t) = V_m \cos(\omega t - \theta)$ and $i(t) = I_m \cos(\omega t - \phi)$ in a circuit element,

- ✓ Voltage leads current by $\theta - \phi$.

- ✓ Average power:

- † $P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$

- ✓ Apparent power: $V_{eff} I_{eff}$ [VA] (ignoring phase difference)

- ✓ Power factor: ratio of average power to apparent power

- † $PF = \frac{P_{avg}}{V_{eff} I_{eff}} = \cos(\theta - \phi)$, where $\theta - \phi$... PF angle

- † $0 \leq PF \leq 1$ ($PF = 1$ for resistive load, $PF = 0$ for purely reactive load)

Power Factor

- Resistor

- ✓ Phase difference, $\theta - \phi = 0^\circ \Rightarrow PF = 1$ (Average power = apparent power)

- ✓ Even in a circuit with inductor and capacitor, it is possible to have equivalent unity power factor.

- Pure reactive component (capacitor or inductor)

- ✓ Phase difference, $\theta - \phi = \pm 90^\circ$ (+ for inductor, - for capacitor) $\Rightarrow PF = 0$

- PF is insensitive to sign of PF angle, $\theta - \phi$.

- ✓ In inductive (유도성) load, current lags voltage ($\theta - \phi > 0$): Lagging PF 지상 역률

- ✓ In capacitive (용량성) load, voltage leads current ($\theta - \phi < 0$): Leading PF 진상 역률

Complex Power 복소 전력

• Complex power, \mathbf{S}

$$\mathbf{S} = \mathbf{V}_{eff} \mathbf{I}_{eff}^* = V_{eff} I_{eff} e^{j(\theta - \phi)} = P_{avg} + jQ$$

† $\text{Re}\{\mathbf{S}\} = P_{avg}$ [W] and $\text{Im}\{\mathbf{S}\} = Q$ [VAR] (reactive power, 무효 전력)

† Reactive power represents the flow of energy back and forth to the load.

$$\dagger P_{avg} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$\dagger Q = V_{eff} I_{eff} \sin(\theta - \phi)$$


$$\dagger |\mathbf{S}| = V_{eff} I_{eff}$$

Various Powers


Quantity	Symbol	Formula	Units
Average power	P_{avg}	$V_{eff} I_{eff} \cos(\theta - \phi)$	Watt [W]
Reactive power	Q	$V_{eff} I_{eff} \sin(\theta - \phi)$	VAR, volt-ampere-reactive
Complex power	\mathbf{S}	$P_{avg} + jQ$ $V_{eff} I_{eff} \angle(\theta - \phi)$ $\mathbf{V}_{eff} \mathbf{I}_{eff}^*$	VA, volt-ampere
Apparent power	$ \mathbf{S} $	$V_{eff} I_{eff}$	VA

Power Triangle

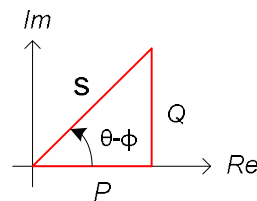- Complex power, $\mathbf{S} = P_{avg} + jQ$



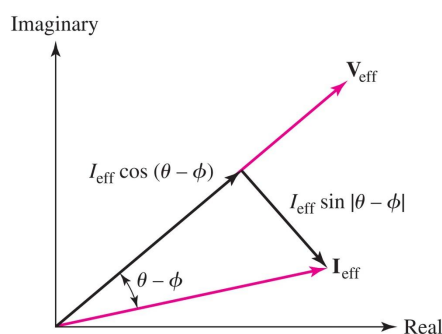- Phasor diagram of \mathbf{V}_{eff} and \mathbf{I}_{eff}



회로이론-2. 11. AC Power Analysis

11-17

Phasor Factor Correction

- Consumer wants an electric power supply with **constant average power and constant voltage**.

✓ $P_{avg} = V_{eff} I_{eff} \cos(\theta - \phi)$

✓ Lower PF \Rightarrow larger current is required

† Large current requires large current-carrying capacity.

† Large current often causes increased loss in the electrical power transmission and distribution system.

† Thus, large current asks **increased cost** to power supplying company.

✓ Almost all electric facilities are inductive and thus have lagging PF.

✓ In order to improve the PF, we connect a capacitor in parallel to the load (**역률 개선용 진상 condenser**)

회로이론-2. 11. AC Power Analysis

11-18

Phasor Factor Correction

1. Calculated the required reactive power

$$\checkmark \tan \theta_o = \frac{Q}{P_{avg}} \text{ and } \tan \theta_n = \frac{Q-Q_c}{P_{avg}}$$

$$\checkmark Q_c = P_{avg}(\tan \theta_o - \tan \theta_n)$$

2. Connect a capacitor in parallel



$$\checkmark \mathbf{S} = \mathbf{VI}^* = \mathbf{V}(\mathbf{I}_1 + \mathbf{I}_2)^* = \mathbf{S}_1 + \mathbf{S}_2 \text{ (complex power after correction)}$$

$$\checkmark \text{Choose } \mathbf{S}_2 = \mathbf{S} - \mathbf{S}_1 = -jQ_c \text{ (pure capacitive)}$$

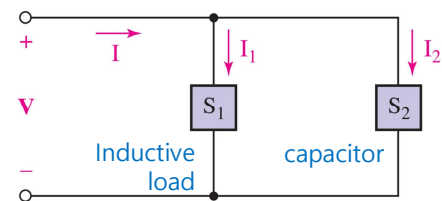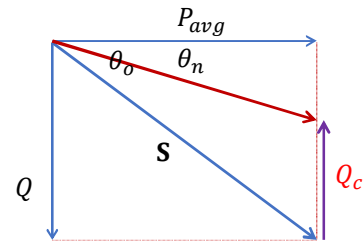3. Find the capacitance

$$\checkmark \mathbf{S}_2 = \mathbf{VI}_2^* = \mathbf{V} \cdot \left(\frac{\mathbf{V}}{\mathbf{Z}_2}\right)^* = \frac{V_{eff}^2}{\mathbf{Z}_2^*} \text{ (assume } \mathbf{V} = V_{eff} \angle 0^\circ)$$

$$\checkmark \mathbf{Z}_2 = \frac{V_{eff}^2}{\mathbf{S}_2^*} \text{ or } \frac{1}{j\omega C} = \frac{V_{eff}^2}{jQ_c} \quad C = \frac{P_{avg}(\tan \theta_o - \tan \theta_n)}{\omega V_{eff}^2}$$



Phasor Factor Correction

- **Example 11.10** Industrial customer is operating a 50 [kW] induction motor at a lagging PF of 0.8 with $V_{eff} = 230$ [V rms].

$$\checkmark \text{Old PF, } 0.8 \Rightarrow \theta_1 = \cos^{-1} 0.8 = 36.9^\circ \text{ and new PF, } 0.95 \text{ lagging} \Rightarrow \theta_n = \cos^{-1} 0.95 = 18.195^\circ$$

$$\checkmark \text{Complex power to motor, } \mathbf{S}_1 = P_{avg} + jQ_1 = 50 + j \frac{P_{avg}}{0.8} \sin \theta_1 = 50 + j37.5$$

$$\checkmark \text{Complex power to corrected load,}$$

$$\dagger \mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 = P_{avg} + jQ_n = 50 + j \frac{P_{avg}}{0.95} \sin \theta_n = 50 + j16.43$$

$$\checkmark \text{Complex power to correct, } \mathbf{S}_2 = \mathbf{S} - \mathbf{S}_1 = -j21.07 \text{ [kVA]}$$

$$\checkmark \text{Capacitance, } \mathbf{Z}_2 = \frac{V_{eff}^2}{\mathbf{S}_2^*} = \frac{230^2}{j21.07} = -j2.51$$