

# Chapter 4. Node & Mesh Analysis Methods

1. Node Analysis
2. Mesh Analysis


회로이론-1. 4. Node & mesh analysis

4-1

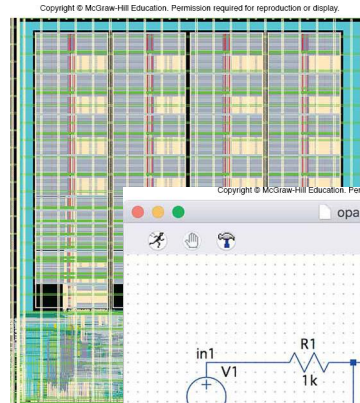
## Circuit Analysis

- As circuits get more complicated, we need an organized method of applying KVL, KCL, and Ohm's Law
  - ✓ Nodal analysis assigns voltages to each **node**, and then we apply **KCL**.
  - ✓ Mesh analysis assigns currents to each **mesh**, and then we apply **KVL**.

Deep learning processor with  $2 \times 10^7$  transistors



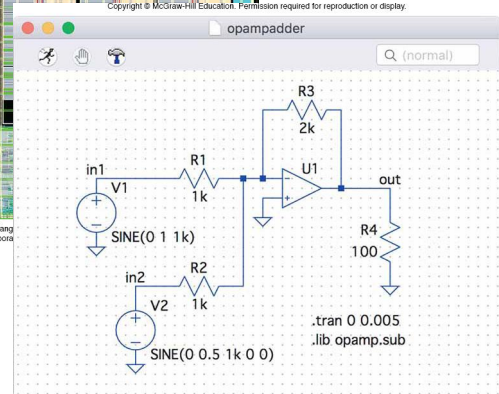(Source: Jingcheng Wang Integrated Circuits Labors)



회로이론-1. 4. Node & mesh analysis

4-2

# Nodal Analysis Method



1. Identify nodes in the circuit.

✓ 3 nodes in the circuit

2. Choose a reference node.

✓ 가장 많은 branch를 연결하는 node를 기준 node로 선택

3. Assign node voltages to all node.

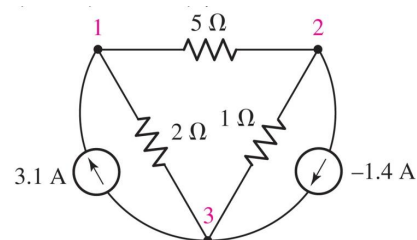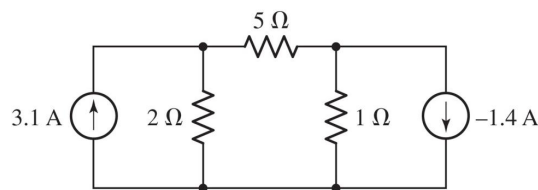


회로이론-1. 4. Node & mesh analysis

4-3

# Nodal Analysis Method

4. Compute the branch voltage and branch current in terms of the node voltages.

5. Apply KCL to each node.

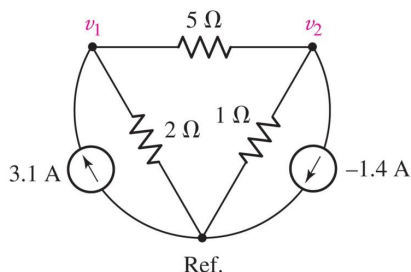

Node-1:

$$\frac{v_1}{2} + \frac{v_1 - v_2}{5} = 3.1$$

Node-2:

$$\frac{v_1 - v_2}{5} = v_2 - 1.4$$

$$\begin{bmatrix} 0.7 & -0.2 \\ 0.2 & -1.2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 3.1 \\ -1.4 \end{bmatrix}$$

$$v_1 = \frac{\begin{vmatrix} 3.1 & -0.2 \\ -1.4 & -1.2 \end{vmatrix}}{\begin{vmatrix} 0.7 & -0.2 \\ 0.2 & -1.2 \end{vmatrix}} = \frac{-4}{-0.8} = 5, \quad v_2 = \frac{\begin{vmatrix} 0.7 & 3.1 \\ 0.2 & -1.4 \end{vmatrix}}{\begin{vmatrix} 0.7 & -0.2 \\ 0.2 & -1.2 \end{vmatrix}} = 2$$

회로이론-1. 4. Node & mesh analysis

4-4

## Nodal Analysis Method


- Example 4.1 Find  $i$ .

$$\text{Node-1: } \frac{v_1}{10} + \frac{v_1 - v_2}{15} = 2$$

$$\text{Node-2: } \frac{v_2}{5} = \frac{v_1 - v_2}{15} + 4$$

$$i = \frac{v_1 - v_2}{15}$$

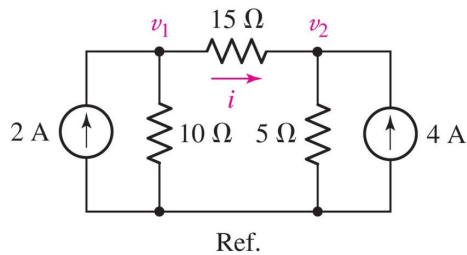
$$\begin{bmatrix} 5 & -2 \\ -1 & 4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 60 \\ 60 \end{bmatrix}$$



## Nodal Analysis Method

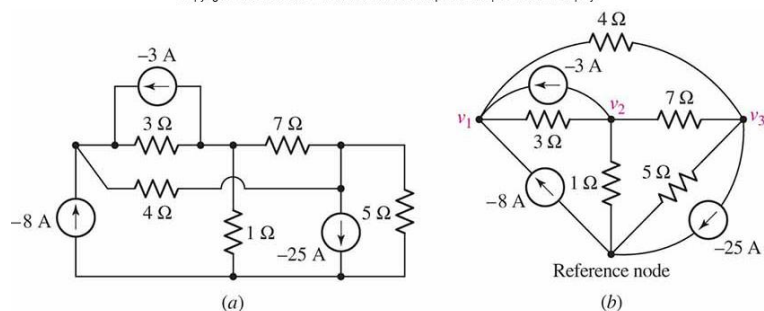- Example 4.2 Find node voltages.

Copyright © McGraw-Hill Education. Permission required for reproduction or display.



$$\begin{bmatrix} .5833 & -.3333 & -.25 \\ -.3333 & 1.4762 & -.1429 \\ -.25 & -.1429 & .5929 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix}$$

# Nodal Analysis Method

- Circuit with dependent sources

- **Example 4.3** Find the power supplied by the dependent source.


✓ Since the node analysis is based on KCL, dependent current source is easy to handle.

✓ Node-1:  $v_1 - v_2 + \frac{v_1}{2} = 15$

✓ Node-2:  $v_2 - v_1 + \frac{v_2}{3} = 3i_1$

✓ 보조 방정식:  $i_1 = \frac{v_1}{2}$
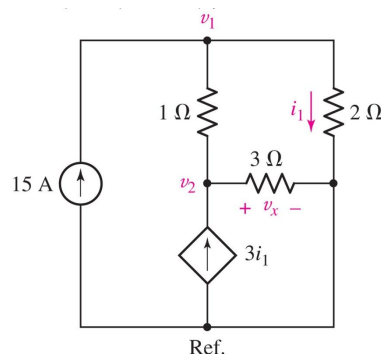
$$\begin{bmatrix} 3 & -2 \\ -15 & 8 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 30 \\ 0 \end{bmatrix}$$



회로이론-1. 4. Node & mesh analysis

4-7

# Nodal Analysis Method


- When a circuit has a voltage source:

✓ Hard to determine the branch current on the voltage source.

✓ One way is to assign a branch current, introducing a new variable.

✓ The other is to introduce the **supernode** and apply KCL on the supernode.

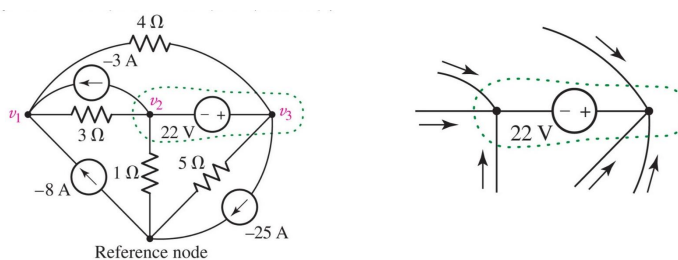† Supernode는 전압원 branch의 양쪽 node를 하나의 node로 구성한 가상의 node



회로이론-1. 4. Node & mesh analysis

4-8

## Nodal Analysis Method: Supernode

✓ Node-2:

$$\frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} = 14$$


✓ 3-4 supernode:

$$\frac{v_3 - v_2}{2} + v_4 + \frac{v_4 - v_1}{2.5} = 0.5v_x$$

✓ 보조 방정식:

$$v_3 - v_4 = 0.2v_y, \quad v_y = v_4 - v_1, \quad \text{and} \quad v_x = v_2 - v_1$$
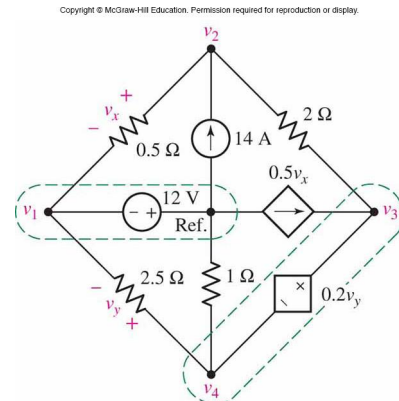
$$\begin{bmatrix} -2 & 2.5 & -0.5 & 0 \\ 0.1 & -1 & 0.5 & 1.4 \\ 1 & 0 & 0 & 0 \\ 0.2 & 0 & 1 & -1.2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 14 \\ 0 \\ -12 \\ 0 \end{bmatrix}$$




## Mesh Analysis

- A mesh is a loop which does not contain any other loops within it.


✓ In mesh analysis, we assign **mesh currents** and solve using KVL.

✓ This circuit has four meshes:

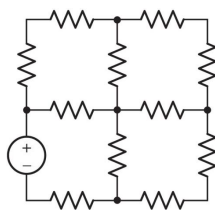

## Mesh Analysis

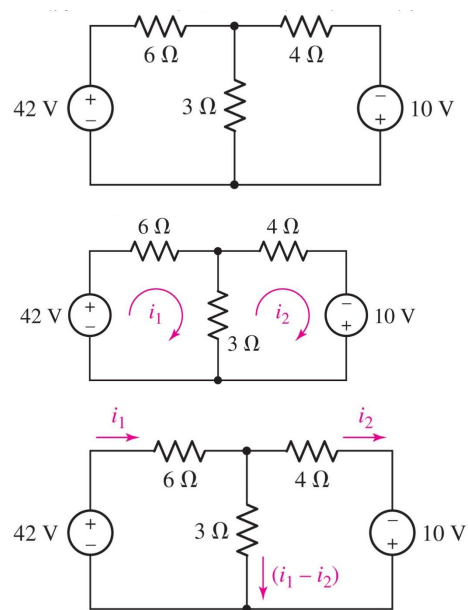1. Identify meshes in the circuit.
2. Assign mesh currents to all mesh.
3. Express the branch current and branch voltage in terms of mesh currents.  
 ▽ Branch current와 mesh current 간의 차이점과 관계를 정확하게 이해해야 한다.
4. Apply KVL to each mesh.



회로이론-1. 4. Node & mesh analysis

4-11

## Mesh Analysis


▽ Mesh-1

$$-42 + 6i_1 + 3(i_1 - i_2) = 0$$

▽ Mesh-2

$$-3(i_1 - i_2) + 4i_2 - 10 = 0$$
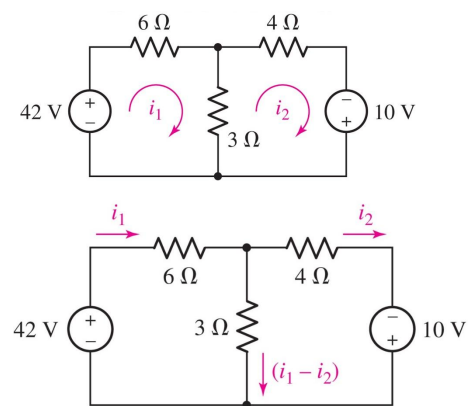
$$\begin{bmatrix} 9 & -3 \\ -3 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 42 \\ 10 \end{bmatrix}$$



회로이론-1. 4. Node & mesh analysis

4-12

## Mesh Analysis

- **Example 4.7** Find the power supplied by the 2[V] source.


✓ Mesh-1

$$4i_1 + 2(i_1 - i_2) = 2 + 5$$

✓ Mesh-2

$$2(i_2 - i_1) + 5i_2 + 1 = -2$$
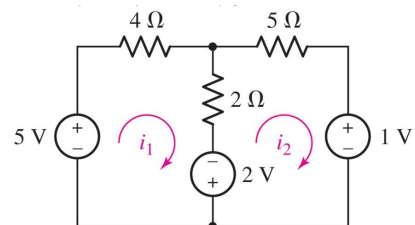
$$\begin{bmatrix} 6 & -2 \\ -2 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 7 \\ -3 \end{bmatrix}$$



## Mesh Analysis

- **Example 4.8** Find mesh currents.

✓ Mesh-1

$$(i_1 - i_2) + 6 + 2(i_1 - i_3) = 7$$


✓ Mesh-2

$$2i_2 + 3(i_2 - i_3) + (i_2 - i_1) = 0$$

✓ Mesh-3

$$3(i_3 - i_2) + i_3 + 2(i_3 - i_1) - 6 = 0$$
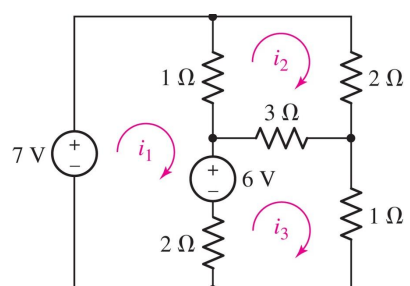
$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$



## Mesh Analysis

- Mesh analysis on a circuit with dependent sources

- **Example 4.9** Find  $i_1$ .


✓ Mesh-1

$$4(i_1 - i_2) + 2i_1 + 3 = 0$$

✓ Mesh-2

$$4(i_2 - i_1) + 4i_2 = 5 + 4i_1$$
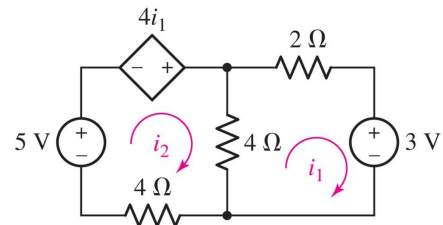
$$\begin{bmatrix} 8 & -8 \\ -6 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -5 \\ 3 \end{bmatrix}$$



## Mesh Analysis: Supermesh


- Mesh analysis on a circuit with current sources

✓ Hard to determine the branch voltage on the current source.

✓ One way is to assign a branch voltage, introducing a new variable.

✓ The other is to introduce the **supermesh** and apply KVL on the supermesh.

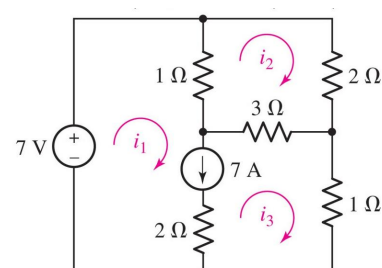† Supermesh는 전류원 branch를 공유하는 한 쌍의 mesh를 하나의 mesh로 구성한 가상의 mesh





## Mesh Analysis: Supermesh

### • Example 4.11 Find mesh currents.

✓ Supermesh-1&3

$$(i_1 - i_2) + 3(i_3 - i_2) + i_3 = 7$$


✓ Mesh-2

$$2i_2 + 3(i_2 - i_3) + (i_2 - i_1) = 0$$

✓ 보조 방정식

$$i_1 - i_3 = 7$$
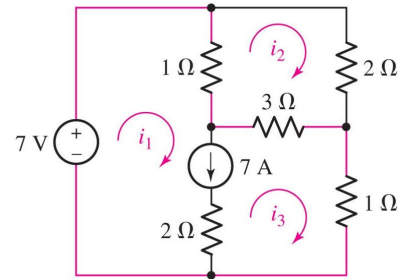
$$\begin{bmatrix} 1 & -4 & 4 \\ -1 & 6 & -3 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 7 \\ 0 \\ 7 \end{bmatrix}$$



## Mesh Analysis: Supermesh

### • Example 4.12 Find mesh currents.


✓ There is no way to compute branch voltages on current sources.

✓ Mesh-2

$$2i_2 + 3(i_2 - i_3) + (i_2 - i_1) = 0$$

✓ 보조 방정식
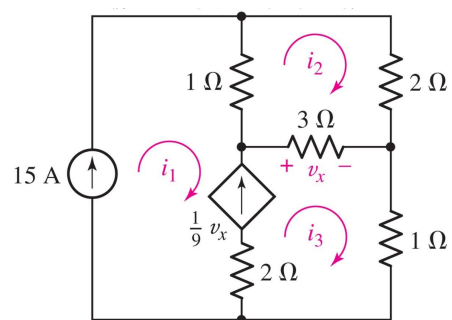
$$i_1 = 15, \frac{v_x}{9} = i_3 - i_1, \text{ and } v_x = 3(i_3 - i_2)$$



## Node or Mesh: How to choose?

- 선택 기준

- ✓ Fewer equations

- † Circuit with voltage sources: Mesh analysis

- † Circuit with current sources: Node analysis

- ✓ Your preference

